

Electronics

029:128

Lecture Notes

John Goree

2007

First lecture begins w/ discussion  
of syllabus, lab



## "Ground"

- as a convention,  
zero volts = "ground potl."
- it's a large body capable  
of accumulating or losing  
lots of electrons
- examples:
  - water pipe stuck into soil
  - metal enclosure of battery-  
powered circuit
- symbols:



## "Voltage Drop"

= difference in potential  
between two points

## "Bias"

= a voltage, usually DC

DC vs. AC

DC	$\approx 10 \text{ Hz}$
audio freq.	$\approx 20 \text{ kHz}$
RF (radio freq)	$\approx 100 \text{ kHz}$




for RF, potl varies along length of wire, due to short  $\lambda$

DC, audio: potl is nearly constant along a wire

Electrical Power

60 Hz	N. America
50 Hz	Euro, Asia

Amplitudes for AC:

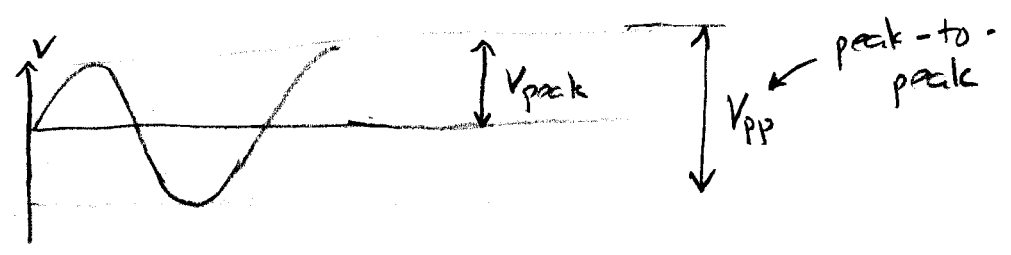

$$V_{rms} = \frac{1}{\sqrt{2}} V_{peak}$$

$$\uparrow V_{peak} = \frac{1}{2} V_{PP}$$


# About schematic diagrams

an early goal of course: learn to read them




wire


assume elec potl is uniform along wire

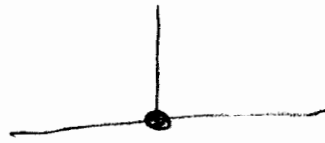


node = connected

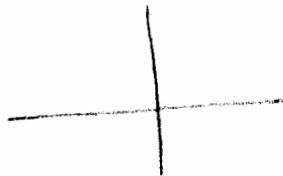

not connected

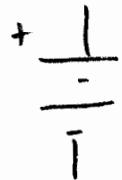

battery

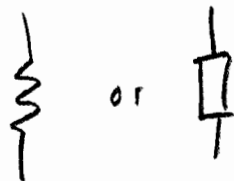


or


resistor



capacitor


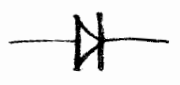


diode

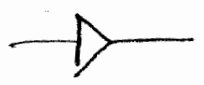



amplifier

### Conventions for drawing schematics:

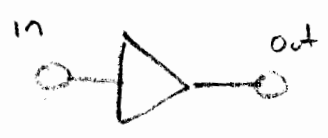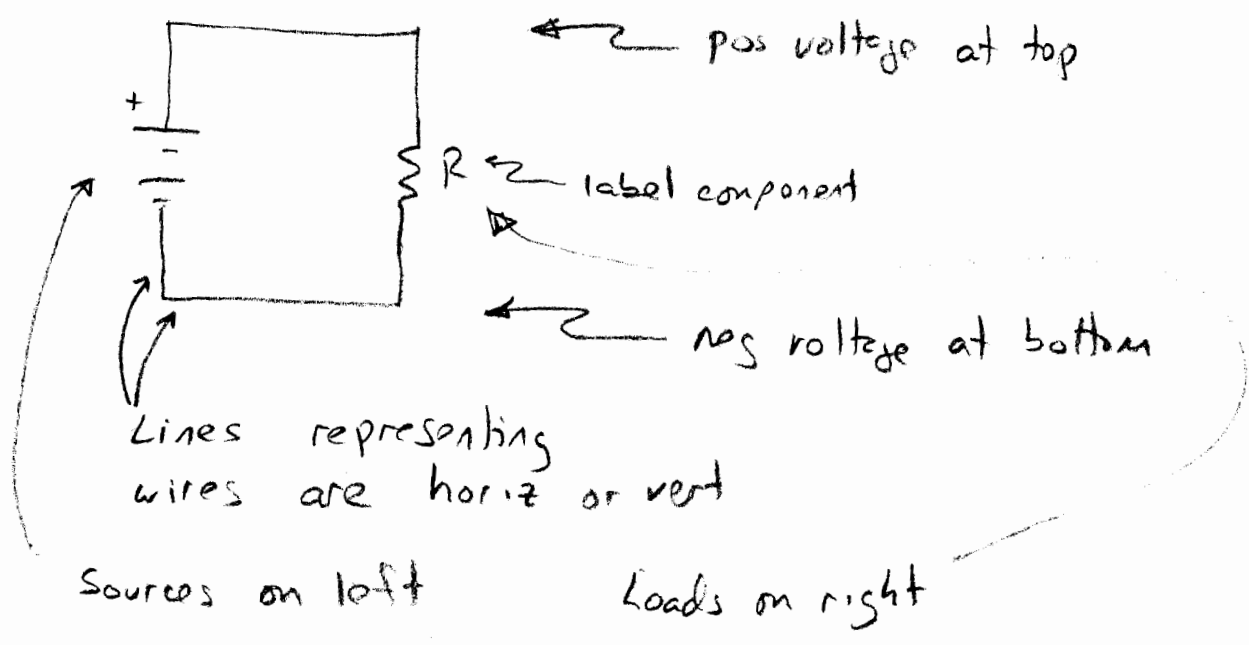

signals flow left to right

4 way nodes:

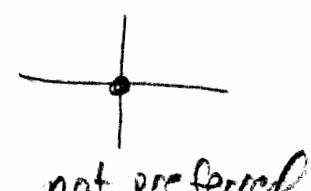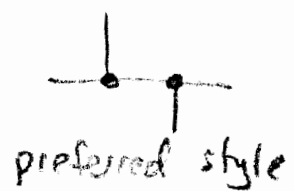

# Statistical Treatment of Exptl. Data

(7)

here, we interrupt presentation of electronics fundamentals to review errors, so that you can do lab 1

## Terminology

- "measurement errors" are  $\pm$  uncertainties
- two kinds:

"systematic" - e.g. thermometer is not calibrated

"random" - unpredictable variations in expt

- if you repeat measurement 10 times, you get 10 different results

- examples of causes:

- unpredictable fluctuations in temperature, illumination
- observer judgment in estimating tenths of smallest division

- small systematic errors → high "accuracy"
- .. random .. → .. "precision"

Concepts for errors

- If you make only one measurement, it is sometimes hard to say whether errors are random or systematic
- here, "errors" does not refer to difference between theory & exptl. measurement
- in electronics, measurement errors typically occur in analog quantities (voltage, time, etc.) not in logic levels True & False

How to determine error

- usually, see mfg. specifications for instrument.
- ex. multimeter, Hertz -  
 mfg. spec 1.00% reading + 3 LSD  
 (cont.) ↑  
"least signific. digit"



(9)


your reading 60.12 Hz

↑  
LSD is 0.01 Hz

your uncertainty:  $0.60 + 3 \times 0.01$   
 $= 0.63$

you report:  $60.12 \pm 0.63$  Hz

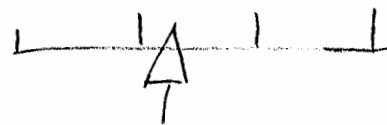- sometimes, with analog measurements, operator's opinion of how nearly he/she can read position of needle or waveform compared to scale



- seldom, jitter in indicated value of digital display

Propagation of Errors ← use in some labs, not all

↑ How you determine ± uncertainty of a calculated quantity

ex. you measure  $V_{out} \pm \Delta V_{out}$ ,  $V_{in} \pm \Delta V_{in}$   
you calculate  $A = \frac{V_{out}}{V_{in}}$

you find uncertainty  $\Delta A$  using prop of errors:

$$(\Delta A)^2 = (\Delta V_{in})^2 + (\Delta V_{out})^2$$

generally: if  $Q$  is calculated from  $a$  &  $b$   
then  $\Delta Q$  uncertainty is calculated:



$$(\Delta Q)^2 = \left(\frac{\partial Q}{\partial a} \Delta a\right)^2 + \left(\frac{\partial Q}{\partial b} \Delta b\right)^2$$

note that errors add thru their squares

back to Foundations

concepts:

series / parallel

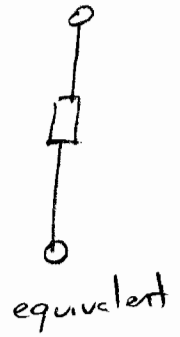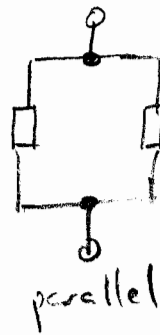


for resistors:

series:  $R_{equiv} = R_1 + R_2$

parallel:  $" = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$

direction of current flow

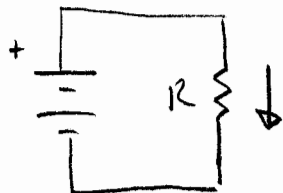

positive current flows  
 from more pos. voltage  
 to more neg. "

# Ohm's Law

$$\boxed{V = IR \quad I = V/R}$$

where

V = voltage "drop" across resistor

I = current thru "

Ohm's Law is empirical  
↑ good for some materials  
not all

## Resistors


- Three parameters:
  - resistance R
  - tolerance typ. ±5%
  - power rating ← don't exceed this, or you burn it up; see this
- Power dissipated

$$\boxed{P = IV}$$

$$\boxed{P = I^2 R = V^2/R} \text{ for a resistor}$$

some schematic symbols


switches

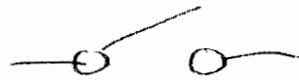

SPST


single pole single throw

(use for on-off)

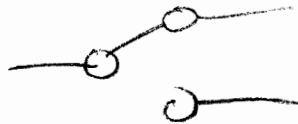


SPDT

(use to select A or B)

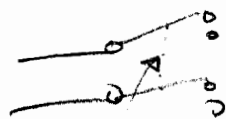


DPST

"ganged"

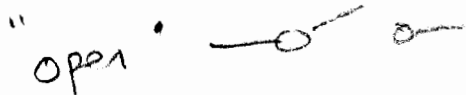


"normally open" bush button

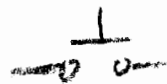


terminology


"open circuit"

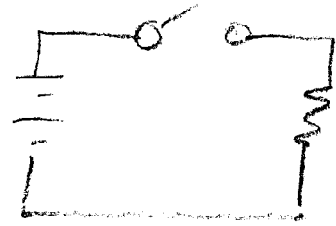

"closed circuit"

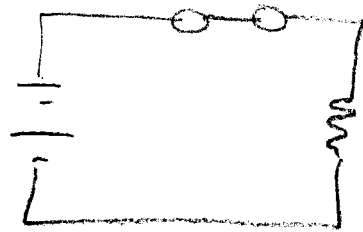

"short circuit"

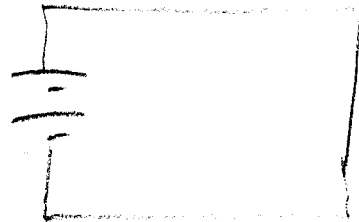

# Kirchoff's Laws


The physics behind circuit analysis

## Voltage Law

(conservation of energy for an electron)

"Sum of Voltage Drops around a closed loop is zero"

ex.

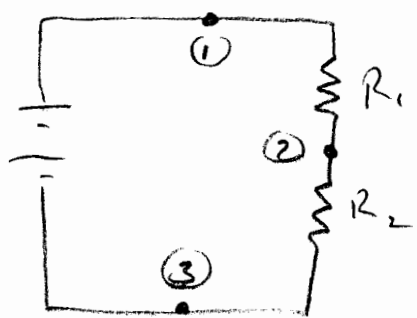


$$\underbrace{(V_2 - V_1)}_{\text{voltage drop across } R_1} + \underbrace{(V_3 - V_2)}_{\text{drop across } R_2} + \underbrace{(V_1 - V_3)}_{\text{drop across battery}} = 0$$

to use law, choose either cw or ccw, then go around complete loop

Current Law

(conservation of charge)

"Sum of currents into a node is zero"

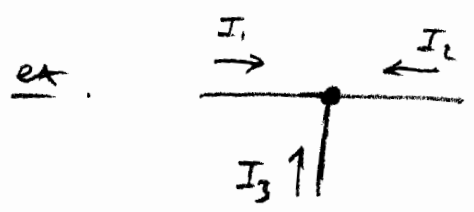

$$I_1 + I_2 + I_3 = 0$$


to use, first decide (arbitrarily) which direction represents positive current, arrows in example indicate choice of direction for pos. current flow



# Voltage Dividers

two resistors in series

leave on board

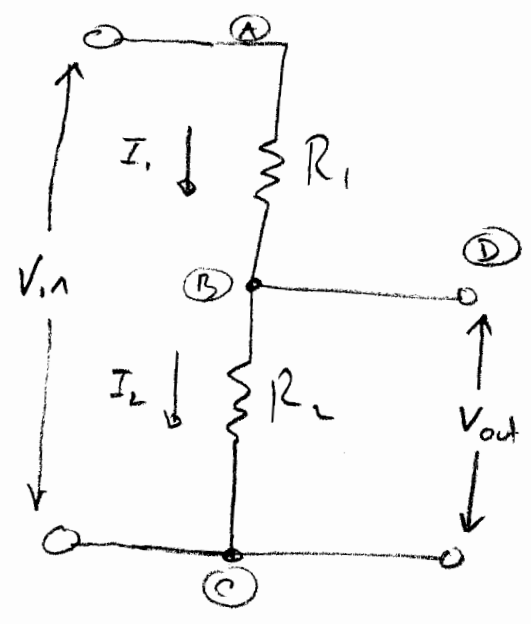

Find  $\frac{V_{out}}{V_{in}}$

\* Method of analysis (you'll see this repeated for many circuits)

- 1<sup>st</sup> identify components, nodes, loops
- 2<sup>nd</sup> write their rules, in algebraic form.
- 3<sup>rd</sup> combine, to eliminate variables, yielding desired quantity

1<sup>st</sup> components  $R_1, R_2$   
 nodes  $(B), (C)$   
 loops none shown

2<sup>nd</sup> for  $R_1$ , Ohms Law  $\frac{V_A - V_B}{R_1} = I_1$

for  $R_2$ , ...  $\frac{V_B - V_C}{R_2} = I_2$



note my convention:  
 positive current assumed  
 to flow from top to bottom



for node  $(B)$ : Kirch. Curr. Law  
 $\Rightarrow$  all current thru  
 $R_1$  must go out  
 either thru  $R_2$  or  
 toward  $(D)$   
 However,  $(D)$  is an open  
 circuit  $\Rightarrow$  no current  
 flows to  $(D)$

$\Rightarrow I_1 = I_2$



$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{R_2}{R_1 + R_2}$$

Voltage Divider

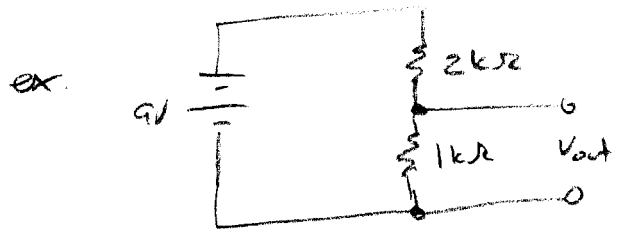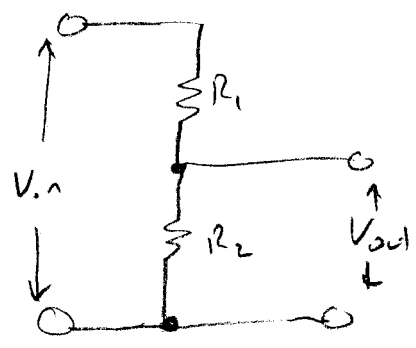

$$V_{out} = 9 \text{ Volt} \frac{1 \text{ k}\Omega}{3 \text{ k}\Omega}$$
$$= 3 \text{ Volt}$$

## Terminology

"Voltage Source" provides fixed  $V_{out}$  regardless of current

"Current Source" " "  $I_{out}$  " " " voltage

voltage source:  $V_{out} = V_{oc}$

- more common
- almost every circuit has one
- battery or power supply

## "sourcing & sinking current"

"Sourcing" if a circuit supplies positive current to a point


"sinking" vice versa

note: "sinking"  $\neq$  resistive dissipation


"offset" = "bias"

- a DC voltage,
- shifts an AC waveform up or down

AC signal

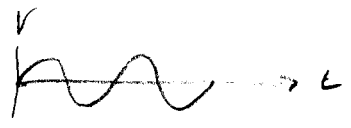

AC signal with DC offset

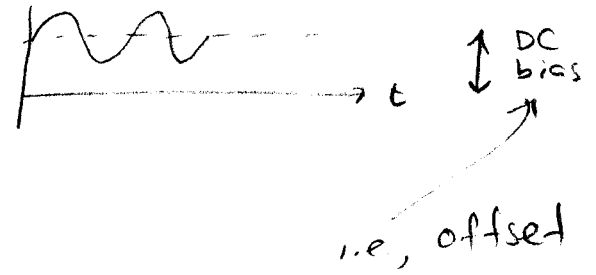

"Gain"

$A_v = \frac{V_{out}}{V_{in}}$  voltage gain

$A_I = \frac{I_{out}}{I_{in}}$  current gain

"Unity Gain"  $\Rightarrow V_{out} = V_{in}$

"decibels"

- to compare ratio of two signals


$$\text{dB} = 20 \log_{10} \frac{\text{amplitude 2}}{\text{amplitude 1}}$$

- often used for gain

ex. ratio is  $1.4 \approx \sqrt{2}$

$$\text{dB} = 20 \log_{10} (1.4)$$

$$= 3 \text{ dB}$$

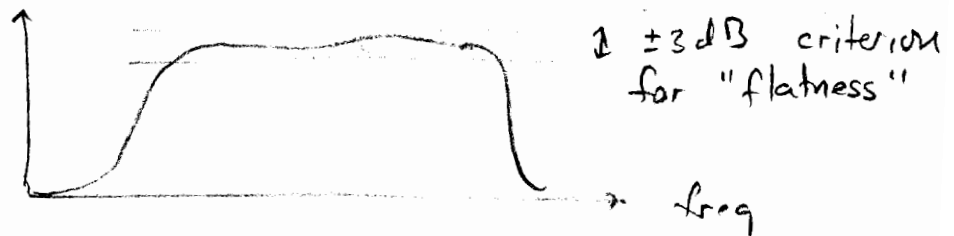
"flatness"

# AC waveform concept

recall  $V_{rms} = \frac{1}{\sqrt{2}} V_{peak} = \frac{1}{2\sqrt{2}} V_{PP}$


## Two components for AC circuits

### transformer

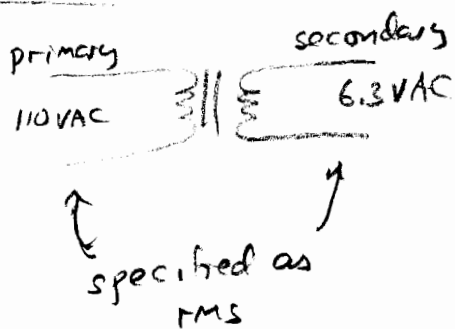

ex. 6.3 VAC transformer  
 input is 110 VRMS → 156 V peak  
 output 6.3 VRMS → 8.9 V peak

### capacitor

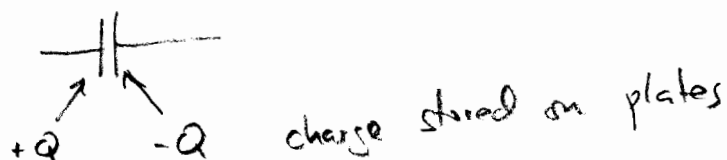

$Q = CV$   
 ↑ potential difference across plates  
 ↑ capacitance in Farads



$$I = \frac{dQ}{dt}$$

$$\rightarrow \boxed{I = C \frac{dV}{dt}}$$

↑ the law for capacitors,  
analogous to  $I = V/R$  for resistors

series

$$\begin{array}{c} \text{---} \\ | \\ \text{---} \\ | \\ \text{---} \\ | \\ \text{---} \end{array} \begin{array}{l} C_1 \\ C_2 \end{array} = \begin{array}{c} \text{---} \\ | \\ \text{---} \\ | \\ \text{---} \end{array} C_{\text{tot}} = \left[ \sum_i C_i^{-1} \right]^{-1}$$


parallel

$$\begin{array}{c} | \\ \text{---} \\ | \\ \text{---} \\ | \\ \text{---} \\ | \\ \text{---} \end{array} \begin{array}{l} C_1 \\ C_2 \end{array} = \begin{array}{c} \text{---} \\ | \\ \text{---} \\ | \\ \text{---} \end{array} C_{\text{TOT}} = \sum_i C_i$$

Lower case symbols

$i$  = AC portion of current waveform

$v$  = voltage waveform

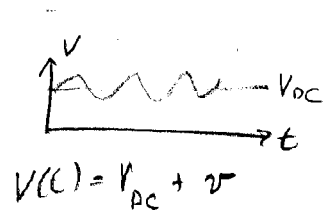

## Math: Complex Numbers

ref. Horowitz Hill Appendix B

$$j^2 = -1$$

$$j = \sqrt{-1}$$

complex no.

$$z = a + bj$$

↑ real part      ↑ imaginary part

complex  
conjugate

$$z^* = a - bj$$

magnitude  
or  
modulus

$$|z| = \sqrt{z z^*}$$

$$= \sqrt{a^2 + b^2}$$

notation

$$a = \operatorname{Re}[z] \quad b = \operatorname{Im}[z]$$

↑ real part of

## Recall Frequencies

$$\omega = 2\pi f$$

↑ units Hz

↑ units  $s^{-1}$

$$f = \frac{1}{\text{period}}$$

# Math: Complex Exponential

$$e^{j\omega t} = \cos \omega t + j \sin \omega t$$

sinusoidal waveform:

$$\begin{aligned} v(t) &= V_0 \cos \omega t \\ &= \operatorname{Re} [V_0 e^{j\omega t}] \end{aligned}$$

derivatives:

$$\frac{d}{dt} e^{j\omega t} = j\omega e^{j\omega t}$$

## Impedance

- a generalized resistance
- allows rewriting law for capacitors so that it resembles Ohm's Law
- symbol  $Z$
- a ratio of voltage / current

## Impedance of Capacitor

recall law  $I = C \frac{dV}{dt}$

AC signal with sinusoidal signal

$$V(t) = V_0 e^{j\omega t}$$

$$\frac{dV}{dt} = j\omega V(t)$$


$$\begin{aligned} \text{impedance } Z &= \frac{\text{voltage}}{\text{current}} \\ &= \frac{V_0 e^{j\omega t}}{j\omega C V_0 e^{j\omega t}} \\ &= \frac{1}{j\omega C} \end{aligned}$$

Impedances

$$Z_c = \frac{1}{j\omega C}$$

$$Z_r = R$$

$$Z_L = j\omega L$$


inductor   
used mainly in  
RF circuits

Ohm's Law for Impedances


$$V(t) = I(t) Z$$

$$I(t) = \frac{V(t)}{Z}$$


series:

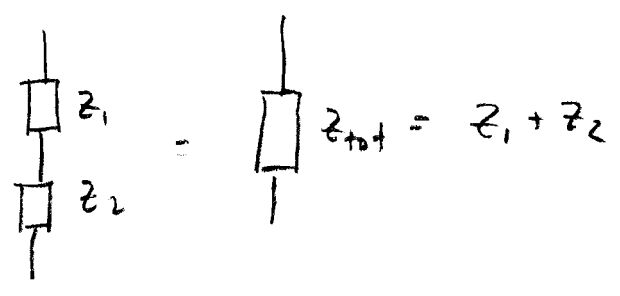

parallel

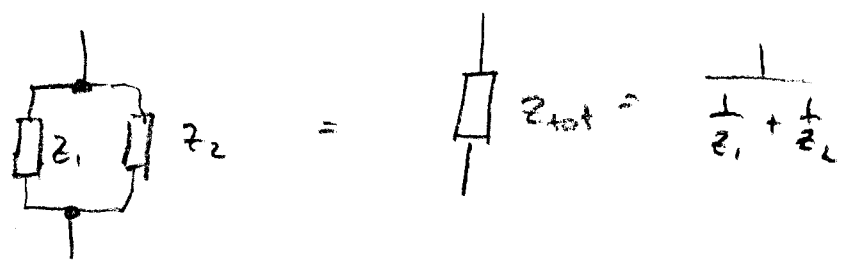

Low Pass Filter

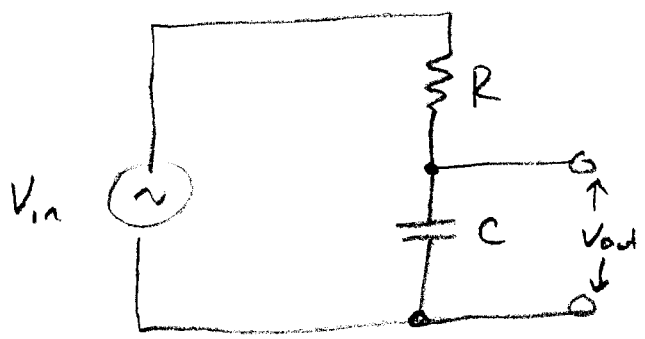

↑  
looks like voltage divider

$$V_{out} = V_{in} \frac{Z_c}{Z_c + Z_R}$$

$$= V_{in} \frac{1/j\omega C}{1/j\omega C + R}$$

$$V_{out} = V_{in} \frac{1}{1 + j\omega RC}$$

↑ ↑  
complex nos.

find amplitude, which is a real no.


$$V_{out}^{ampl} = (V_{out}^* V_{out})^{1/2}$$

↑ real                      ← ↑ complex


$$V_{out} = V_{in} \left[ \frac{1}{(1 + \omega^2 R^2 C^2)} \right]^{1/2}$$

amplitudes (real nos.)

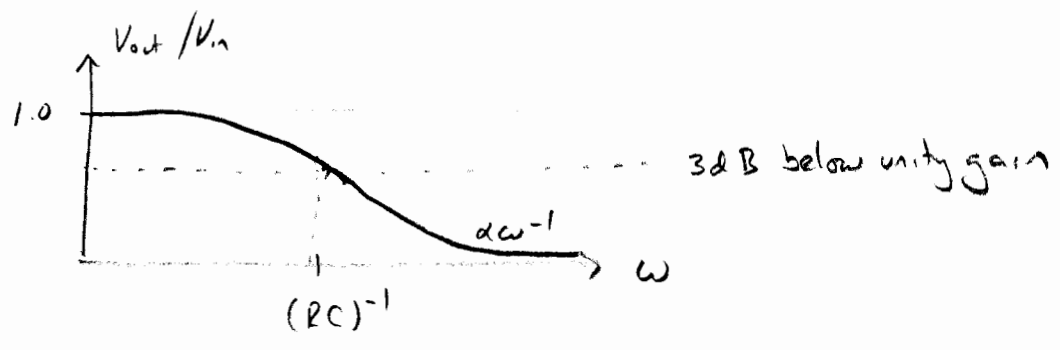"frequency response curve" for Low Pass Filter



## High Pass Filter

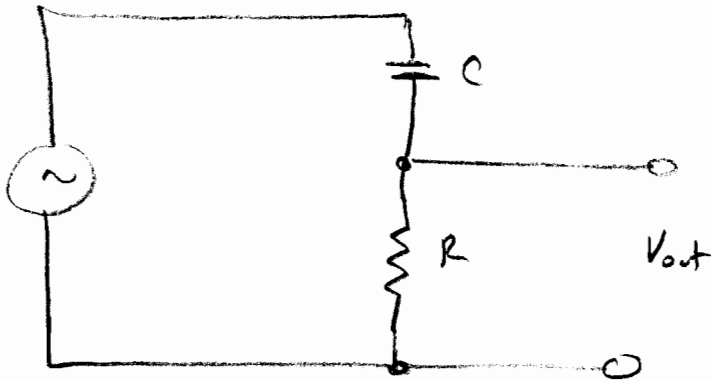

like a voltage divider

$$V_{out} = V_{in} \frac{Z_R}{Z_R + Z_C}$$

$$= V_{in} \frac{R}{R + 1/j\omega C}$$

$$V_{out} = V_{in} \frac{j\omega RC}{j\omega RC + 1}$$

↑            ↑  
complex nos.


find amplitude



$$V_{out} = V_{in} \frac{\omega RC}{(1 + \omega^2 R^2 C^2)^{1/2}}$$

amplitudes  
(real nos.)

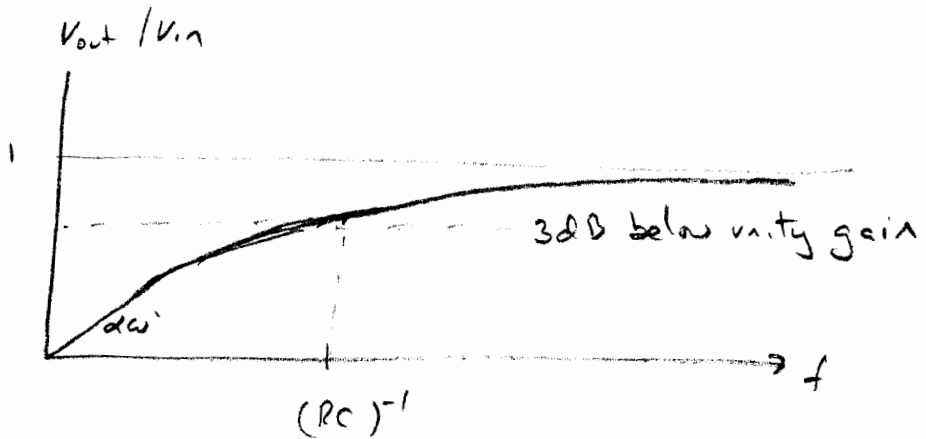freq  
response  
curve  
for  
high-pass



### ex. filter applications

low pass filter: eliminate high freq. noise  
in a transmission of  
human voice w/ signal  $< 7$  kHz

high pass filter: eliminate dc bias in an  
ac waveform


capacitor terminology

"roll-off frequency" of a filter =  $(RC)^{-1}$

"time constant" =  $RC$


"dc-blocking capacitor"

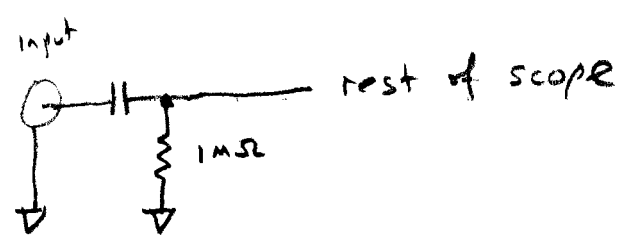- insert a capacitor to remove dc bias
- ex. "AC coupling" of scope:




• also called "capacitive coupling" of a signal

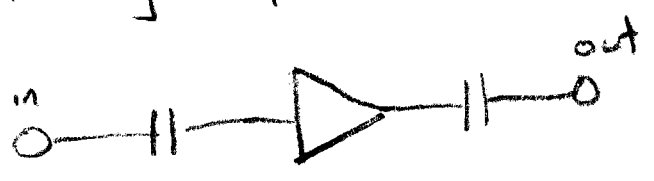- audio amps are often capacitively coupled



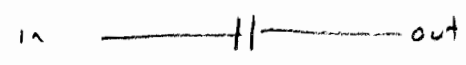
# capacitors & dc bias

- use capacitive coupling to eliminate dc bias



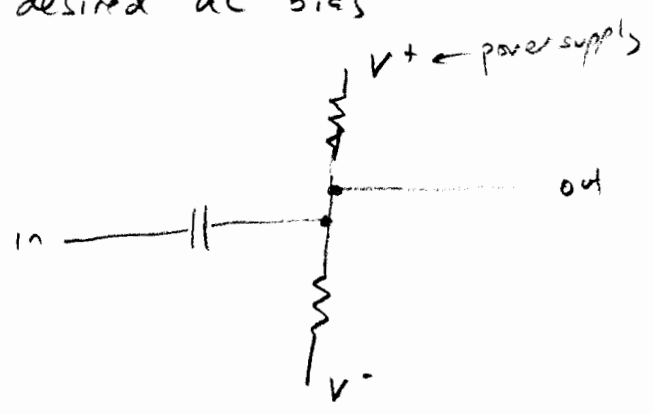- add a voltage divider to apply a desired dc bias



~	~
blocks any	adds
incoming	desired
dc bias	dc bias

terminology


"time domain" · waveform  $V(t)$

"frequency domain" dependence of amplitude on frequency


in lecture, we have considered filters in the "freq. domain"

in lab, you will also measure filter performance in "time domain"

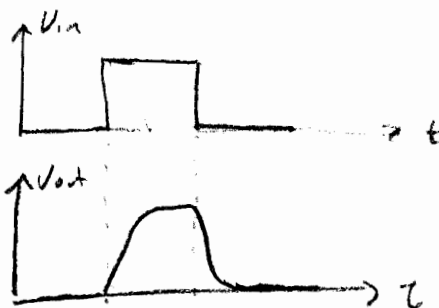ex. time domain, applying a pulse input to a low pass filter




# Diodes

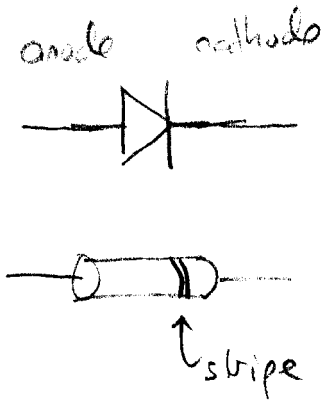

recall: positive current flows  
from a more pos. voltage  
toward a more neg. voltage

diode conduction

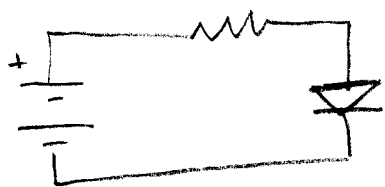

"forward biased" diode  
conducts



"reverse-biased" diode  
doesn't conduct



anode cathode



→ diode can conduct current in this direction

← diode blocks " " " "




current-voltage characteristic of diode

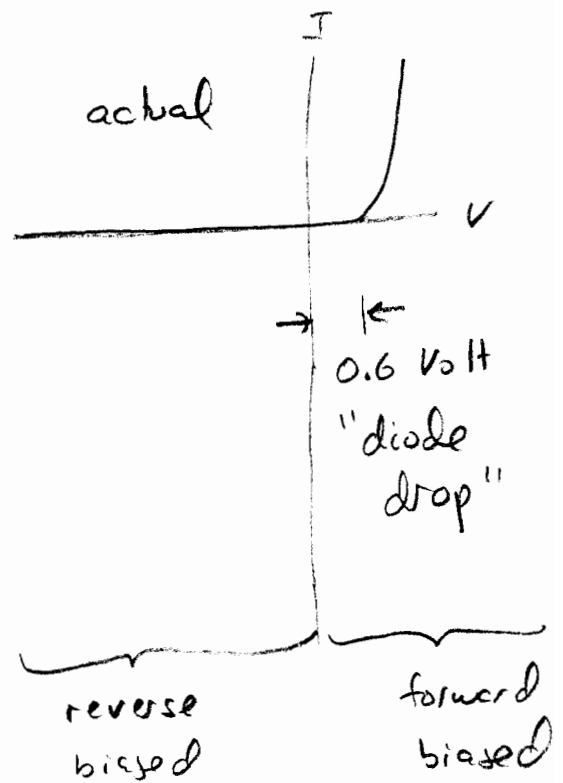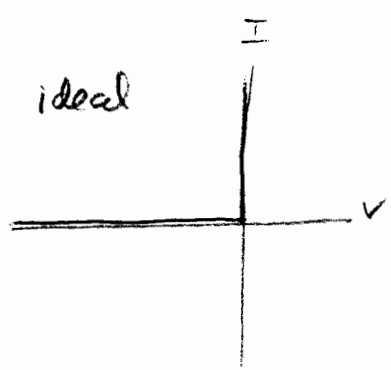


## Diode Applications

- Rectifier (convert AC  $\rightarrow$  DC)

ex. "Half-Wave Rectifier"

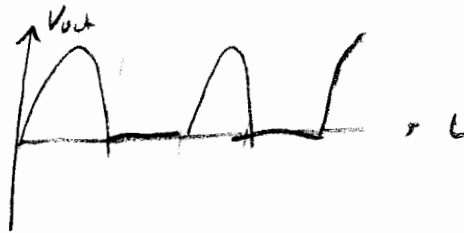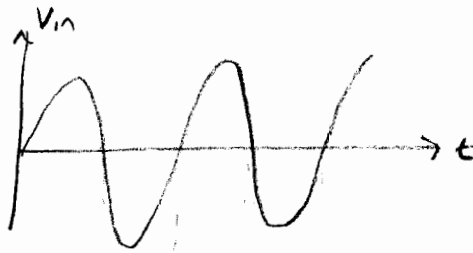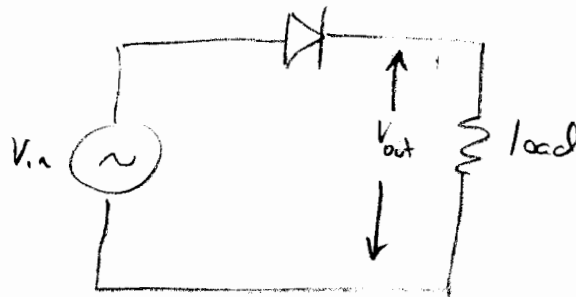

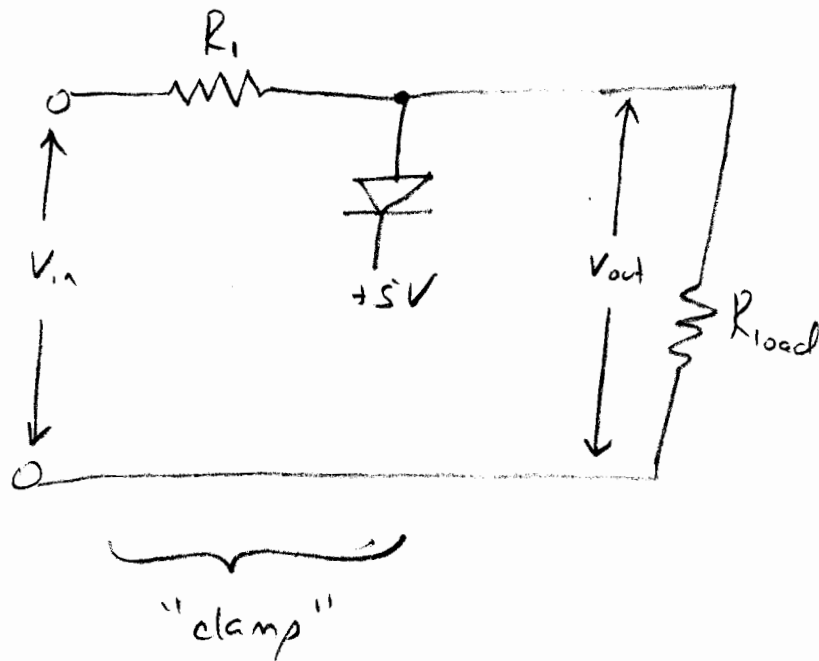
- "Diode Clamp" - prevent output from exceeding a certain positive voltage



- output voltage cannot exceed  $+5V + 0.6V = +5.6V$  because at higher voltages diode would conduct & act like a zero resistance in parallel w/ load
- $R_1$  is a "current limiting resistor" to avoid burning up diode, when diode conducts, typically  $100 - 1k\Omega$




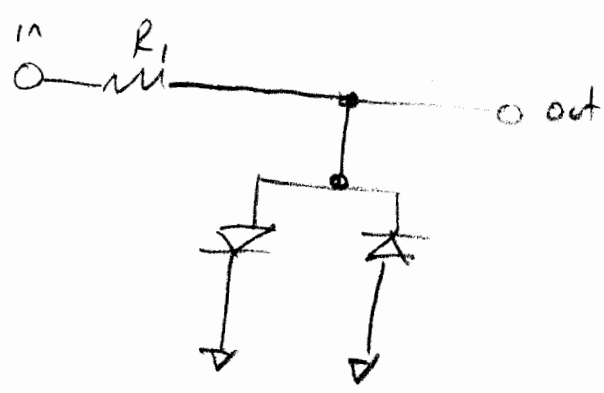• Diode Limiter - prevent output from exceeding pos or neg voltage



prevents output from exceeding  $\pm 0.6$  volt

• How to burn up a diode

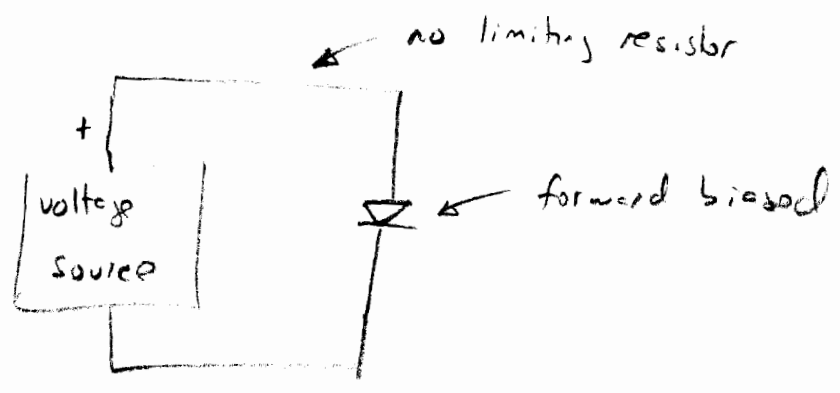


in forward conduction,  
diodes resistance  $\rightarrow 0$

Power dissipated in diode  $\frac{V^2}{0} \rightarrow \infty$

# Types of diodes:

- signal e.g. 1N914 - for low power use
- power - for rectifiers, power supplies


## Zener diode

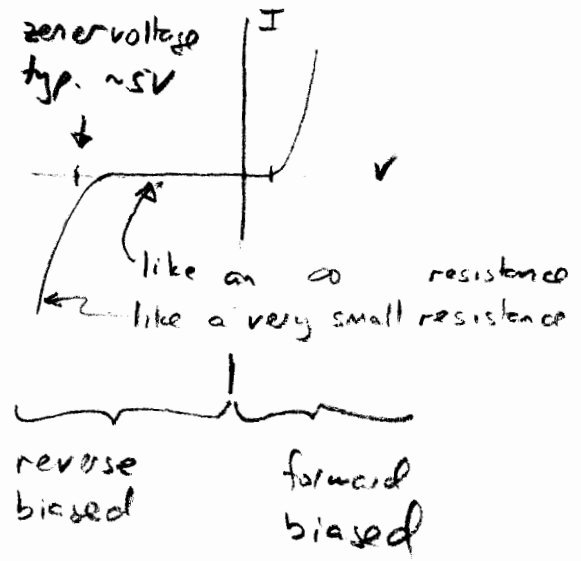

a zener conducts when reverse-biased by more than the "zener voltage"

Zener application : voltage regulator

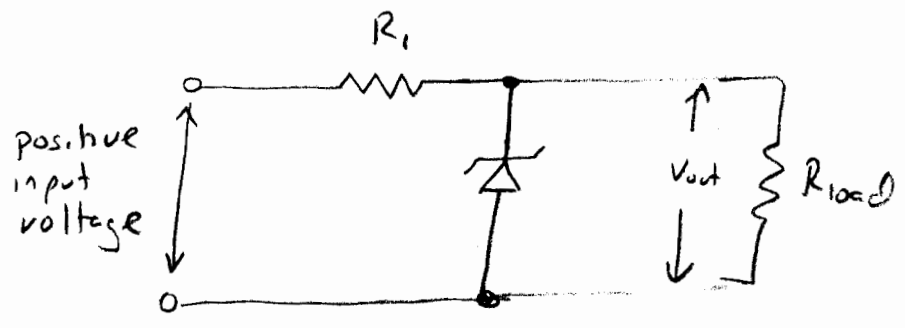↑  
produces a steady output voltage,  
when you apply a larger (unsteady) input



zener is  
reverse  
biased

zeners available for various small zener voltages,  
e.g. 5V