

Transistors

ref. Horowitz & Hill Ch. 2

Prelude

major uses of transistors


- switching
 - amplification
 - other, e.g., current source
- } most common

kinds of electronic switches

analog, power, logic

analog switch

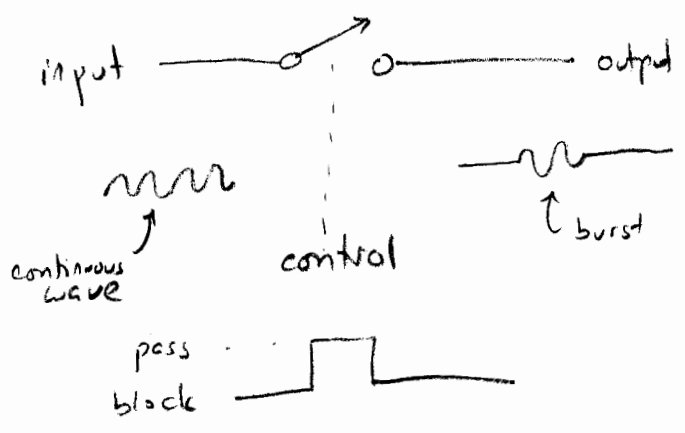either passes or blocks analog signal, ex: TV mute button



power switch

like analog, but for switching
high current, not signals
ex. power on-off for instrument

logic switch

generate full swings between
two power supply voltages, typ. 0 & 5V_{OH}

AND gate




Q = A AND B

inputs		output
A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

↑ 1 = "TRUE" ↔ voltages > 5V
0 = "FALSE" ≅ 0V ↔ " < 0.8V


terminology for amplifiers

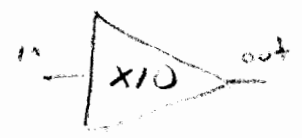


amplifier of gain 10
i.e., 20dB



unity gain amplifier

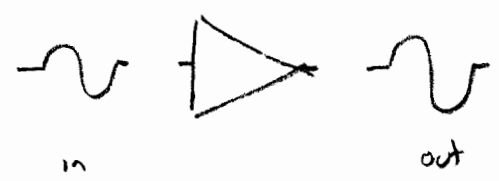

"non-inverting"

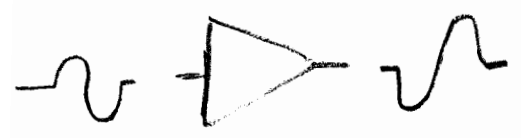


"inverting"

"follower" - like a unity-gain amplifier,
but it might also add a
dc offset to the output waveform

Impedances of Sources & Loads

↑ in lab
you learn to measure

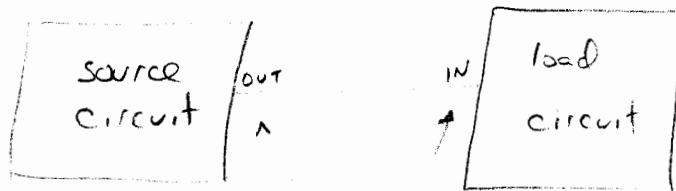often, one connects two circuits together




usually • you prefer $Z_{out} \ll Z_{in}$

- to prevent "loading" of the source circuit, i.e., its output voltage diminishes due to sourcing or sinking lots of current

- ex. source circuit is preamp w/ $Z_{out} = 100\Omega$
load is scope w/ $Z_{in} = 1M\Omega$

radio-frequency applications are exception

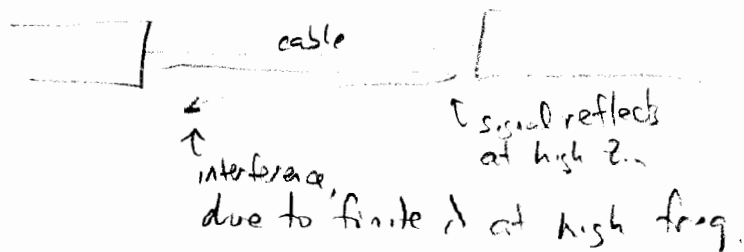
- desire $Z_{out} = Z_{in}$ (typically 50Ω)
- to prevent "reflections" of signal




end of Prelude

Transistors - Basics

BJT = Bipolar Junction Transistor

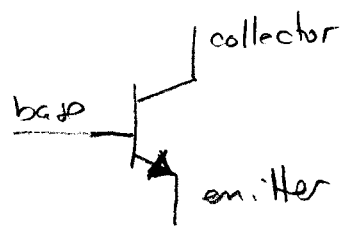


npn
 "not pointing in"

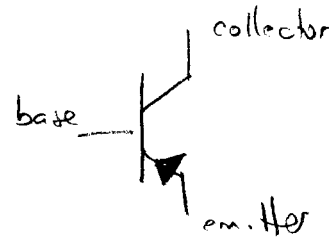

ppn

npn is more common


e.g. 2N2222

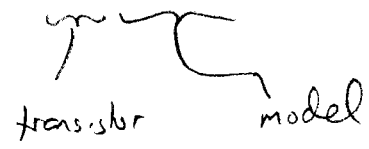

We will use 3 models of transistor:

- "crude"
- "first model"
- "Ebers-Moll" ← a big model, but we will use only one tiny part

notation for transistors

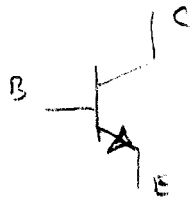

voltages

V_C, V_B, V_E

voltage on transistor terminals C, B, E

V_{CE}, V_{BE}

voltage drop between terminals

V_{CC}

positive power supply voltage

V_{EE}

negative



actually has nothing to do w/ the transistor itself.

currents

I_C, I_B, I_E


current flowing thru that lead of the transistor

Crude Model of Transistor

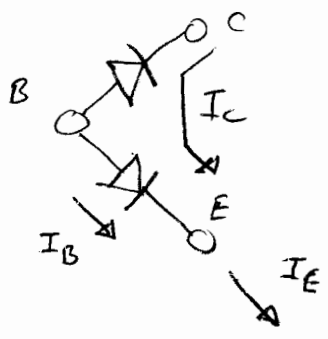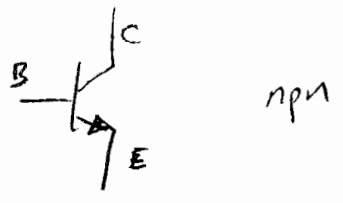

$$I_E = I_C + I_B$$

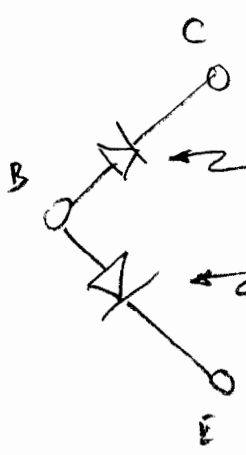- The collector current or the emitter " is usually what you use a transistor for
- The base current is much smaller, and is the input that is used to control I_C or I_E
- I_B is diode conduction, I_C is not



The C-B diode is usually reverse-biased, except in "saturation"

The B-E diode is usually forward biased, except in "cutoff"

Three modes of operation

- saturated (ON)

I_c is big

- cutoff (OFF)

I_c is zero

} used for switches

- active region


^A
 $I_c = h_{FE} I_B$

} used for amplifiers

also called:

- "linear mode of operation"
- "normal"
- "small signal" applications

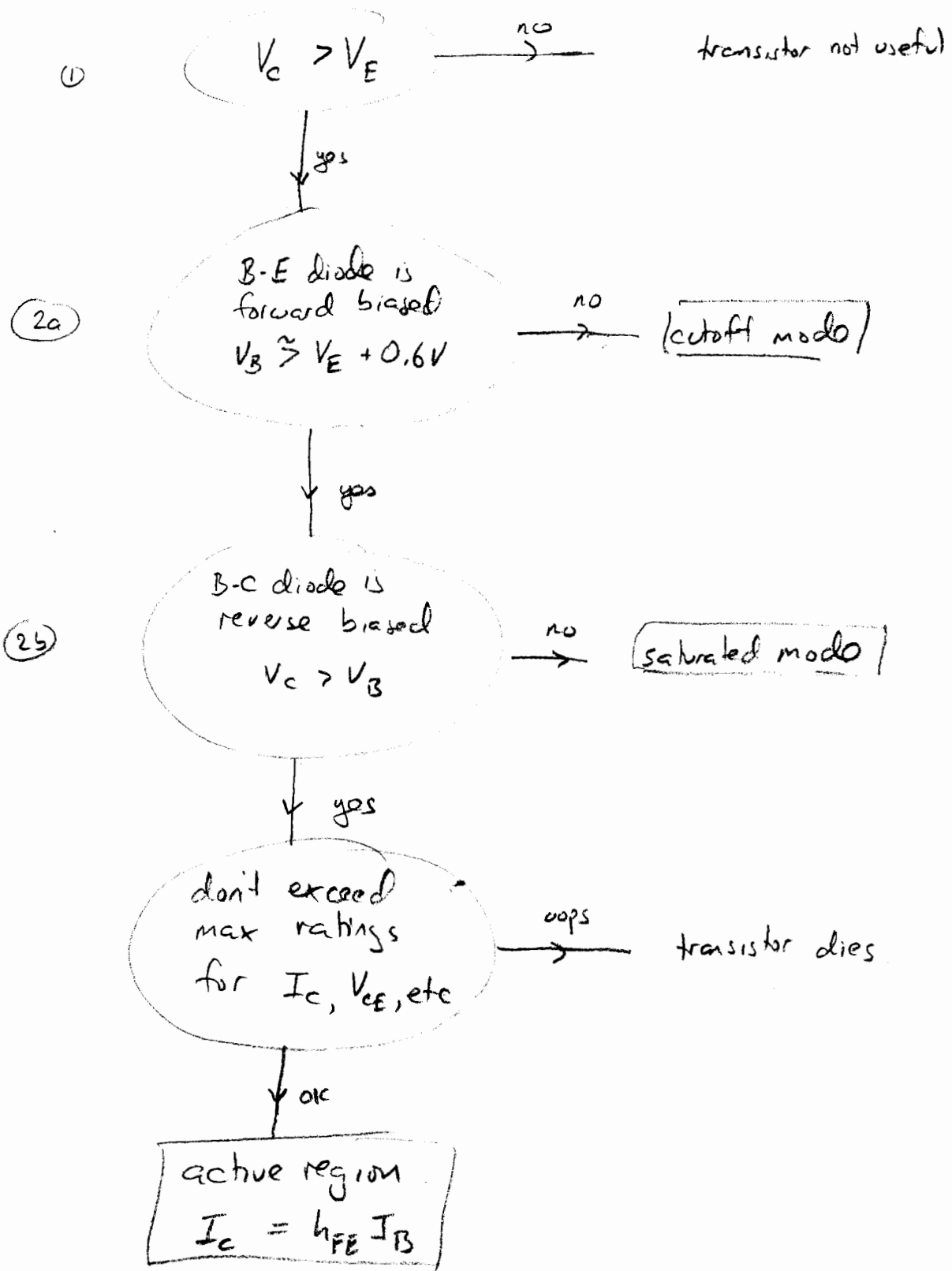
Rules to use transistor in active region condition



Transistor Beta

- $h_{FE} = \beta = \text{"beta"}$
- varies from one transistor to another, mfg. variations
- typically ≈ 100

ex. 2N4400 (Fig. 11, Appendix K, H&H:II)

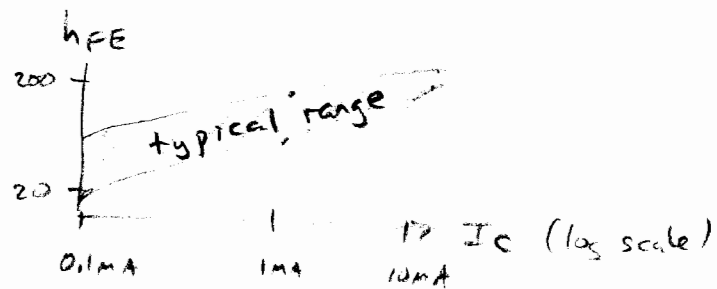


note: • h_{FE} such a poor parameter,
the mfg provides no \pm tolerance


- h_{FE} actually depends slightly on I_C
so $I_C = h_{FE} I_B$ isn't actually
perfectly
linear

- best to design circuits so they
don't depend critically on
 h_{FE} value

more on the "First Transistor Model":

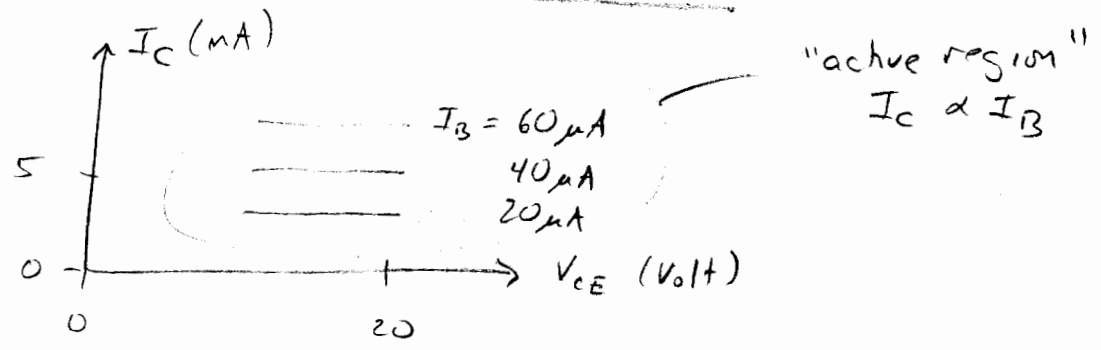


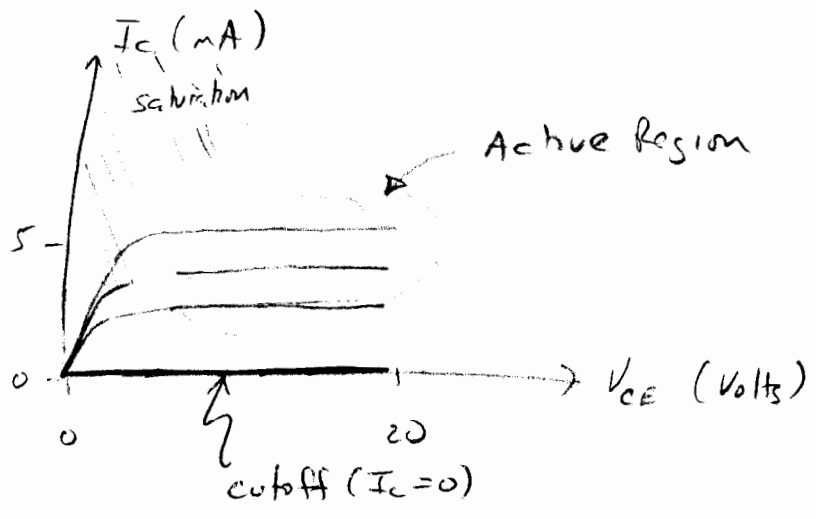↳ a partial graph of NPN characteristics
now add more detail:



Using BJT transistor as a power switch

as in lab #4/

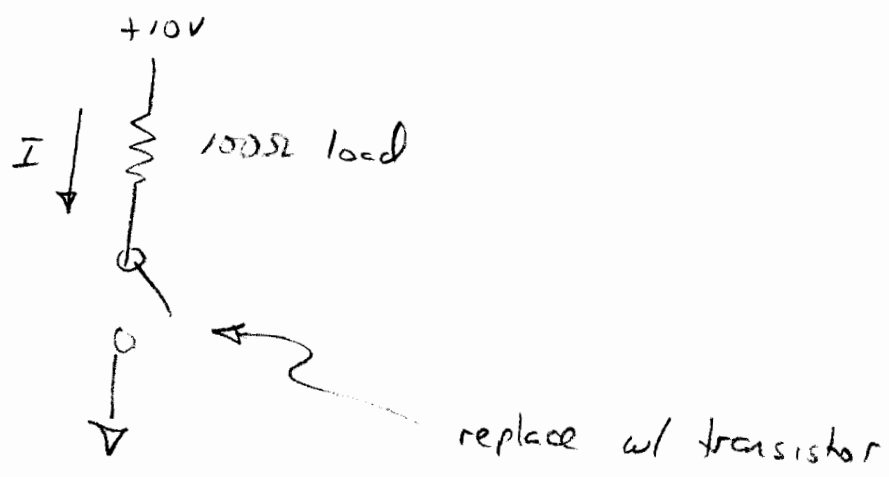

we expect a current of $I = \frac{10V}{100\Omega} = 100\text{ mA}$

↑
ok for BJT
like 2N2222
or 2N4400

if you need to switch lots more current,
it's better to use a "power MOSFET",
later in course.


BJT Transistor Switch

ON = switch closed

use "saturated mode" by applying

lots of base current $I_B \approx 10\text{mA}$


we'll show how to find this

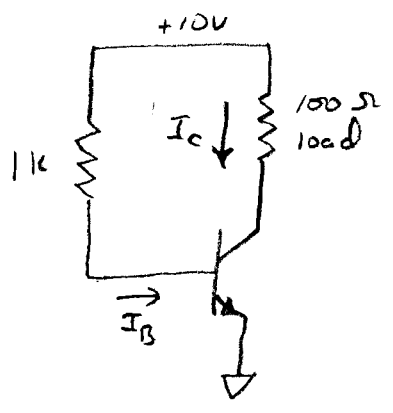


OFF = switch open

use "cutoff mode" by applying zero base current

$$I_B = 0$$

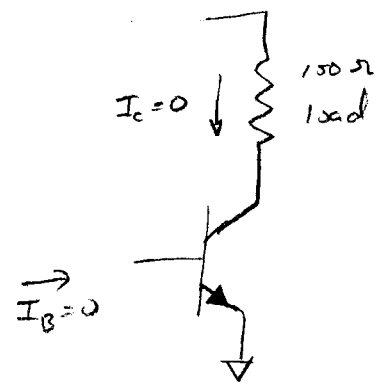

complete circuit

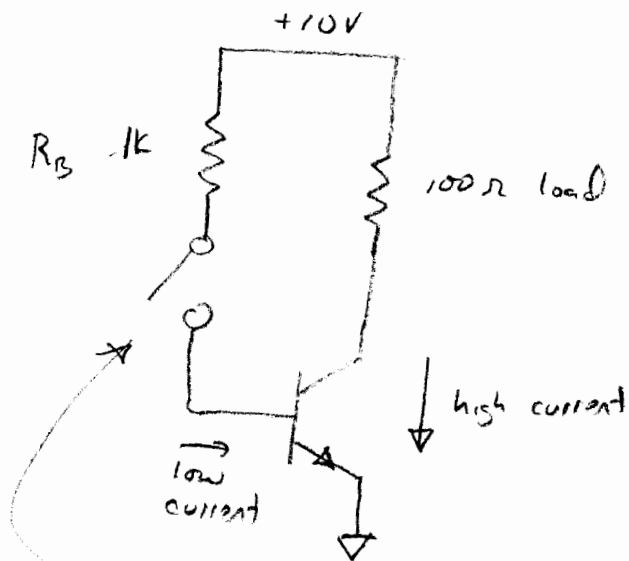

"cold switch" to operate transistor switch

↑ advantages, it allows:

- switching bigger currents than mechanical switch's rating
- Locating control switch remotely, far from high-current circuitry


How to be sure of operating in cutoff mode?

See mfg datasheets, look for hidden label in graph:

ex. 1 2N4400

Appendix K of H&H:11

in Fig. 17 for "ON voltages"

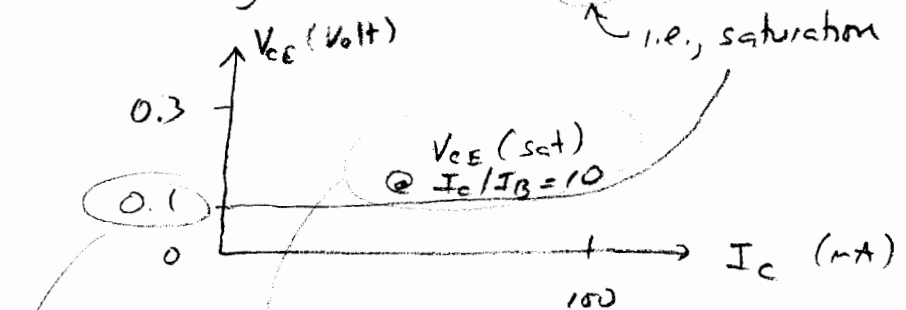

note


this label suggests designing so that $\frac{I_C}{I_B} \cong 10$ to achieve saturation

ex. 2

fairchildsemi.com

datasheet for 2N4400

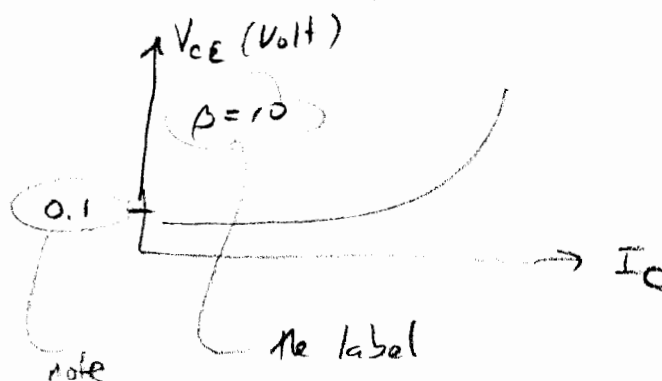graph "Collector - Emitter Saturation Voltage vs. Collector Current"



note

the label

so, from data sheet figures:

- we desire $\frac{I_C}{I_B} \approx 10$ to assure that we operate in the saturated mode
- under these conditions, we expect $V_{CE} \approx 0.1 \text{ V}$

How to analyze:

we want to find R_B

what we know:

2 resistors \Rightarrow use Ohm's Law 2x

transistor in saturation $\Rightarrow \frac{I_C}{I_B} \approx 10$ desired

$V_{CE} \approx 0.1 \text{ V}$ expected

$V_B - V_E \approx 0.6 \text{ V}$ typical

combine these to find R_B

$$R_B = \frac{\text{voltage drop across } R_B}{\text{current thru } R_B}$$

$$= \frac{10\text{V} - V_B}{I_B}$$

$$= \frac{10\text{V} - (V_E + 0.6\text{V})}{I_B}$$

? 0 connected to GND

$$\circ = \frac{9.4\text{V}}{I_B}$$

Find I_B , using $I_C/I_B \approx 10$ desired

$$I_B \approx 0.1 I_C$$

I_c = current thru load resistance of 100Ω

$$= \frac{\text{voltage drop across load}}{100\Omega}$$

$$\approx \frac{10V - V_c}{100\Omega}$$

$$= \frac{10V - (V_c - V_E) - V_E}{100\Omega}$$

$\approx 0.1V$ in saturation
connected to GND

$$\approx \frac{9.9V}{100\Omega}$$

$$\approx 99mA$$

$$\Rightarrow I_B \approx 0.1 I_c \approx 9.9mA$$

↑ plus into ⊙ above

$$R_B \approx \frac{9.9V}{9.9mA} = 949\Omega$$

↑ choose std value $1k\Omega$ within 5%

$$R_B = 1k$$


↑ the std value resistance to choose to assure operating in saturation

end of transistor switch

Now, an amplifier application of BJT

↳ operate BJT in active region

Emitter Follower

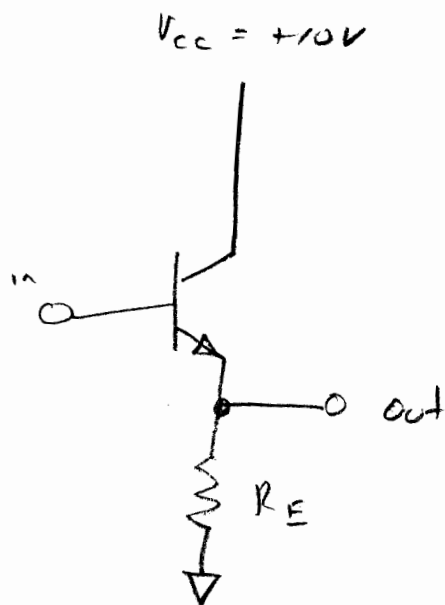

to analyze, we can use:

transistor \Rightarrow use "first model" rules

resistor \Rightarrow Ohm's Law (not needed here, but used later)

$$\begin{matrix} V_E & = & V_B & - & 0.6 & \text{Volt} \\ " & & " & & & \\ V_{out} & & V_{in} & & & \end{matrix}$$

$$\Rightarrow \boxed{V_{out} = V_{in} - 0.6 \text{ Volt}}$$


• this circuit has no voltage gain
(it merely applies a dc bias to the output voltage)

• it can provide current gain,

because it has $\frac{\text{input impedance}}{\text{output "}} > 1$


↑
• you will measure in lab 4
• calculated below

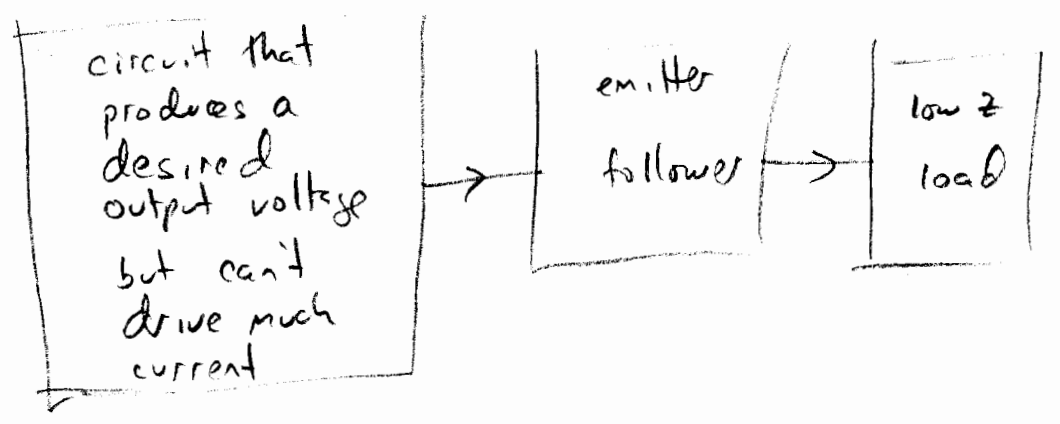useful to: • drive low Z loads
• add to the output of a voltage source to make it "stiffer", i.e., less affected by "loading"



demo multisim: • demonstrate "clipping" with emitter follower
- terminology: "rails"

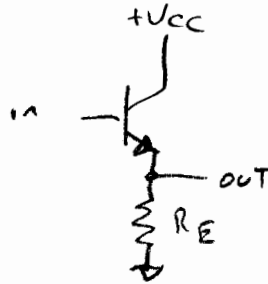Calculate impedances of emitter follower
for ac signals



output impedance Z_{OUT}

easy, because circuit output
is connected directly to
a power supply by a single
resistor R_E

$$\Rightarrow Z_{OUT} = R_E$$

input impedance Z_{IN}

harder

$$\begin{aligned} Z_{in} &= \frac{V_{in}}{I_{in}} \\ &= \frac{V_B}{I_B} \end{aligned}$$

however, here we need an impedance
for ac signals only

recall notation for ac signals:

$$\begin{array}{c}
 \text{if } v(t) = 2V + 5V \sin(\omega t) \\
 \begin{array}{cc}
 \uparrow & \uparrow \\
 \text{dc} & \text{ac} \\
 \text{bias} & \text{amplitude}
 \end{array}
 \end{array}$$

$$v(t) = 5V \sin \omega t$$

↑ lower case denotes ac portion of signal

same for $i(t)$

so we seek

$$Z_{in} \equiv \frac{v_B}{i_B}$$

find a relation between v_B, i_B
 using "first model" rules
 + Ohm's Law

$$I_E = I_C + I_B$$

↑ $I_C = h_{FE} I_B$ in active region

$$\begin{array}{c}
 \uparrow \\
 I_E = \frac{V_B - 0.6V}{R_E} \quad \text{Ohm's Law for } R_E
 \end{array}$$

combine \rightarrow

$$\frac{V_B - 0.6V}{R_E} = (1 + h_{FE}) I_B$$

keep only ac portion

$$\frac{v_B}{R_E} = (1 + h_{FE}) i_B$$

$$\Rightarrow Z_{in} = \frac{v_B}{i_B}$$

$$= (1 + h_{FE}) R_E$$

$L \gg 1$

$$\boxed{Z_{in} \approx h_{FE} R_E}$$

so $Z_{in} \gg Z_{out}$ by factor of $h_{FE} \sim 100$
for em. follower


Transistor Current Source

recall: "current source" provides constant desired value of output current, regardless of the voltage it must output

previous current source we considered (Lab 1)
voltage source + big resistor

Pros: easy

Cons: very sensitive to load impedance

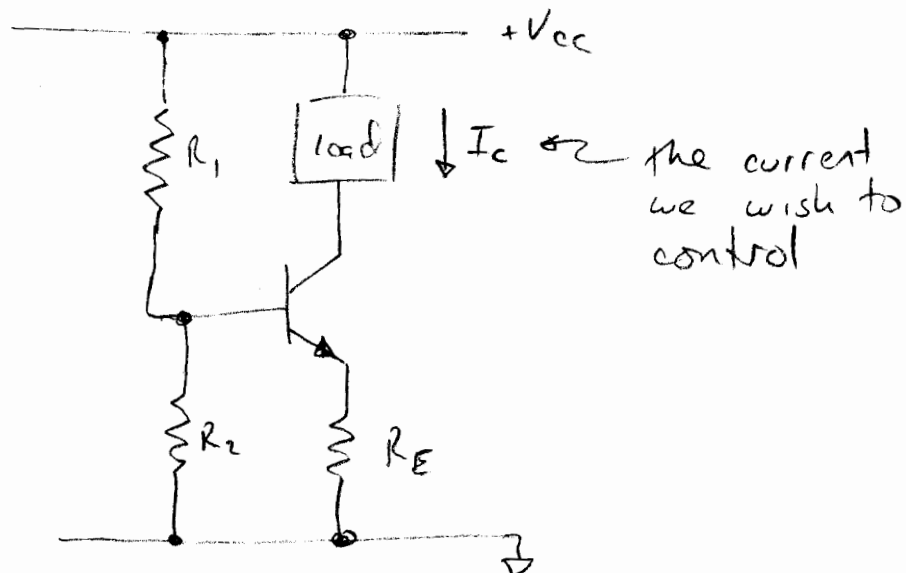

To analyze:

- Transistor "First Model" rules for active region
- Resistors: voltage divider or Ohm's Law

transistor rules:

$$V_E = V_B - 0.6V$$

$$\begin{aligned} I_E &= I_C + I_B \\ &= (1 + h_{FE}^{-1}) I_C \quad \text{in active region} \\ &\cong I_C \end{aligned}$$

Ohm's Law for R_E

$$\begin{aligned} I_E &= \text{current thru } R_E \\ &= \frac{V_E - 0}{R_E} \end{aligned}$$

combine:

$$\boxed{I_C \cong \frac{V_B - 0.6V}{R_E}} \quad \text{output current thru load}$$

voltage divider R_1, R_2 is used to establish V_B

note: good circuit design:

the desired output I_C


depends sensitively only on the supply voltage & resistances, which are good parameters, not on transistor parameters h_{FE} which are not reliable

Common Emitter Amplifier

- a voltage amp, uses BJT in active region
- used mainly for AC signals


Compare to Emitter Follower

Common Emitter

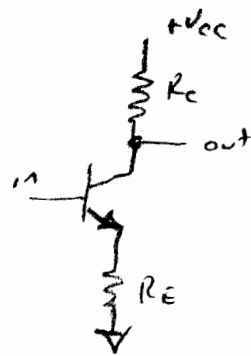

Purpose: voltage gain
 Details: has collector resistor
 output on collector
 $Z_{in} \approx Z_{out}$

Emitter Follower

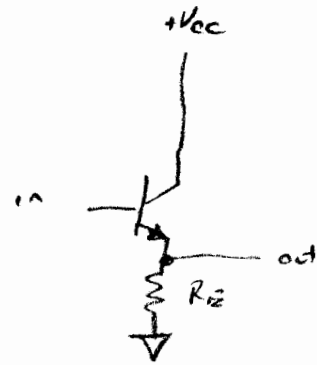

drive a low- Z load
 has none
 output on emitter
 $Z_{in} \gg Z_{out}$

Parameters of interest for amplifiers

70

Gain ← most Important

Maximum Output (Amplitude or Power)

Freq. Response (e.g., gain is constant $\pm 3\text{dB}$
for $20\text{Hz} < f < 20\text{kHz}$)

Z_{in}

Z_{out}

Power Consumption


Analyze common emitter amp to find AC gain $A_v = \frac{v_{out}}{v_{in}}$

First, assess what's involved

- collector resistor \Rightarrow Ohm's Law
- emitter " \Rightarrow " "
- transistor \Rightarrow First Model
- node at output \Rightarrow Kirch. Current Law

↑
here, we ignore if output is connected only to a high Z load

Next, write corresponding equations

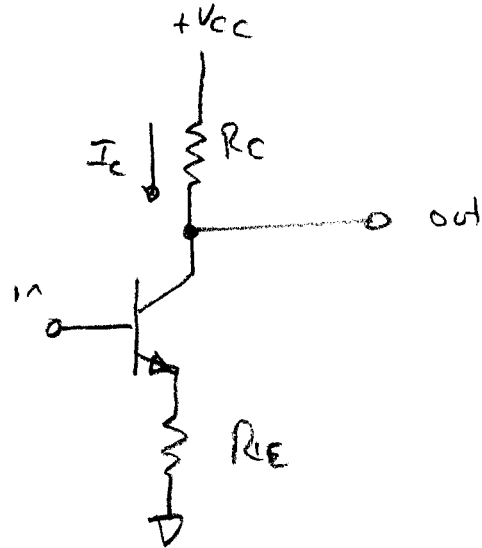

collector resistor: $(V_{CC} - V_{out}) / R_C = I_C$ (1)

emitter: $(V_E - 0) / R_E = I_E$ (2)

transistor (First Model, active region) $V_E = V_B - 0.6 \text{ Volt}$ } (3)
 $\uparrow = V_{in}$

$I_E = I_C + I_B$ (4a)

$= I_C (1 + h_{FE})$ (4b)

then, find V_{out} , V_{in}

$V_{out} = V_{CC} - I_C R_C$ from (1)

$v_{out} = -i_c R_C$ ac part

$$V_{in} = V_B$$

$$= V_E + 0.6 \text{ Volt} \quad \text{from (3)}$$

$$= I_E R_E + 0.6 \text{ Volt} \quad \text{from (2)}$$

$$= I_C (1 + h_{FE}^{-1}) R_E + 0.6 \text{ Volt} \quad \text{from (4)}$$

$$v_{in} = i_c (1 + h_{FE}^{-1}) R_E \quad \text{ac part}$$

Finally, calculate gain for ac signals:

$$A_V = \frac{v_{out}}{v_{in}}$$

$$= - \frac{i_c R_C}{i_c R_E (1 + h_{FE}^{-1})}$$

↑ good that amplifier's gain does not depend on an amplitude like i_c

$$= - \frac{R_C}{R_E (1 + h_{FE}^{-1})}$$

↑ $h_{FE} \approx 100, h_{FE}^{-1} \approx 0.01$

Good circuit design:
The most important circuit parameter (here, gain) depends sensitively only on reliable parameters (here, resistances) not on bad parameters (h_{FE})

Result:


$$A_v \approx - \frac{R_c}{R_E}$$

AC gain of common-emitter amp

↑ note: gain < 0
 ⇒ inverting amp.


multisym demo

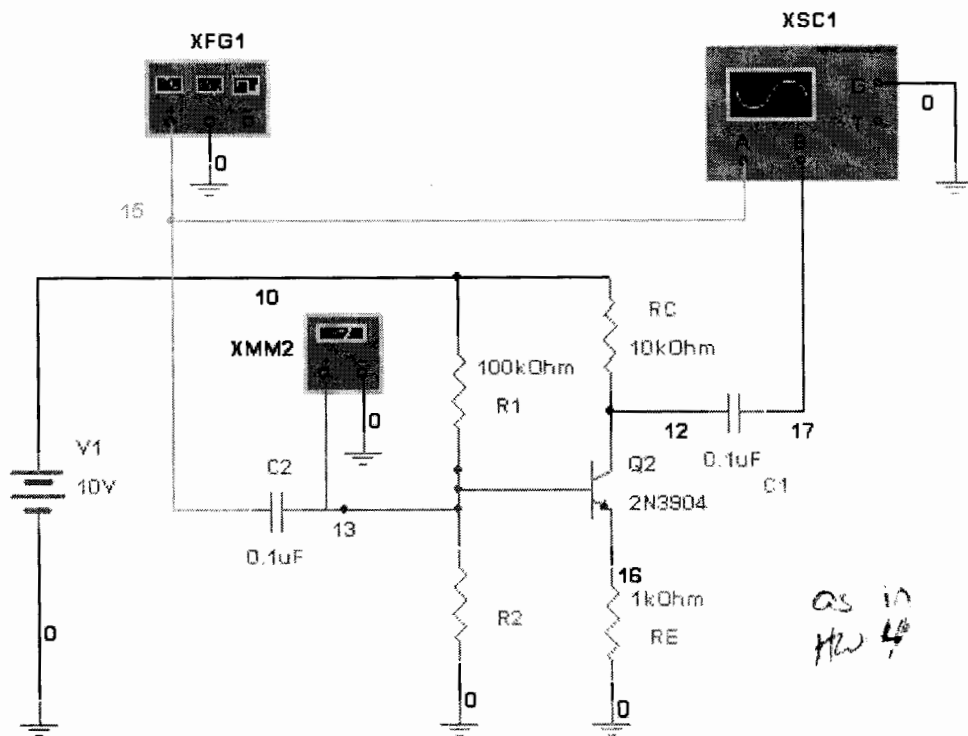
1. demonstrate gain = $-R_c/R_E$ (inverted)
2. .. clipping



demo: clipping of CE amp

- 1) increase input amplitude, observing clipping on output, equally at top & bottom of waveform

 input

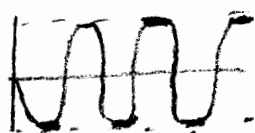

clipping \leftrightarrow flattened waveform at peak

- 2) vary biasing resistor R_2 , observe output clips first on its top, or bottom, not equally on top & bottom, if R_2 is not chosen optimally

(you will do this in the 4)

Common-Emitter Amp -



How to choose biasing resistors

- The biasing resistors establish the dc bias of the transistor's base, which in turn establishes the dc bias of the transistor's emitter & collector.

• Discuss - Which poses a greater problem: the dc bias of base or " " " " collector?

Consider that the output waveform (on the collector) has a larger amplitude than the input waveform on the base, due to gain.

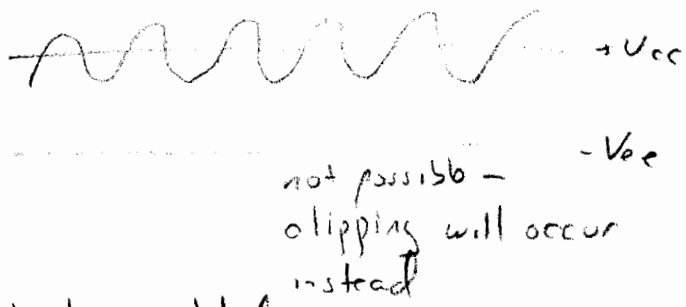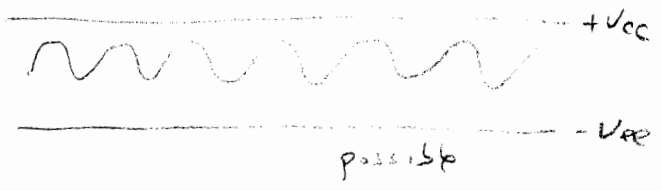
Also consider that all waveforms must fit "within the rails", i.e. between the + V_{cc} - power-supply voltages.



The output amplitude is bigger, so it poses the greater problem to fit its waveform between the rails.

Discussion of bias, continued

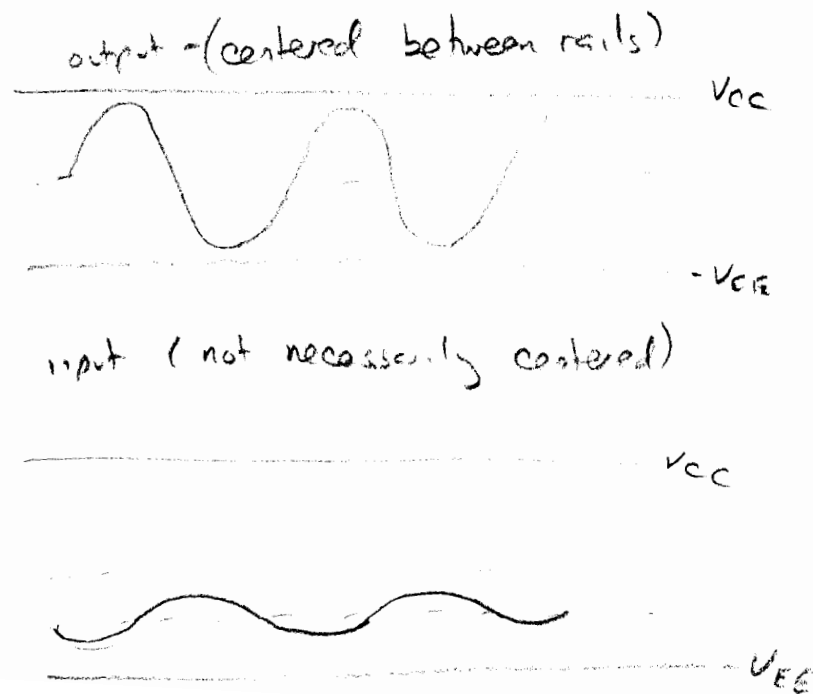- So, given a choice of centering the output waveform or centering the input " between the rails, we choose to center the output waveform so that we make maximum use of the available power supply
- Note that the dc bias on the input (base) and output (collector) are not the same. (This is a common student error.)



Discussion of biasing ~~continued~~

77

- in Hw4, you will calculate value of R_2 to achieve a bias on the base that yields a collector bias that's halfway between the rails.
- how you'll do it (problem 4(a), Hw4) work backwards, including these steps
 - you desire $V_C = \frac{V_{CC} - 0}{2}$ (halfway between rails)
 - Ohm's Law for $R_C \rightarrow I_C$ value
 - Transistor Model $\Rightarrow I_C \approx I_E$ yields I_E value
 - Ohm's Law for $R_E \rightarrow V_E$ value
 - Transistor Model $\Rightarrow V_B \approx V_E + 0.6V$ yields V_B value
 - Voltage divider R_1, R_2 must be designed to provide this desired V_B

You will then use Multisim to test your predicted value of the optimal R_2

Beyond the "First Transistor Model"

"Ebers-Moll" - a big model

- we'll use only one part of it:

Transistor's Intrinsic Emitter Resistance




inside the BJT there is an "intrinsic emitter resistance"

$$r_e \cong \frac{25}{I_c(\text{mA})}$$

25 depends on Temp

ex. if $I_c = 1 \text{ mA}$, $r_e = 25 \Omega$

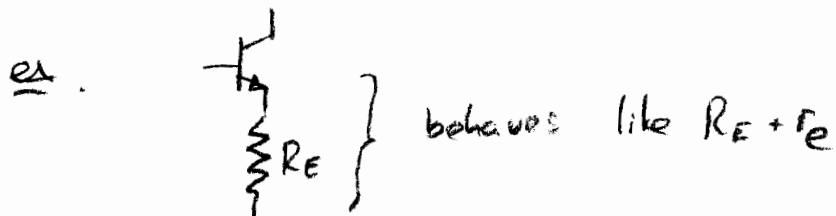This intrinsic emitter resistance appears in series with any components connected to the emitter.



So the gain of a C.E. Amp is really

$$A_v = - \frac{R_c}{R_E + r_e}$$

How to get more gain from a C.E. Amp

• Two obvious ideas are bad:

• make R_E small

(bad because dc, i.e., quiescent current, will depend critically on r_e , temp \Rightarrow unstable).


• make R_c big

(bad because $Z_{out} \approx R_c$ for C.E. Amp, & we prefer a small Z_{out} , as always).

• Clever trick: "emitter-bypass"

you'll do it in the Transistor II lab.

emitter bypass

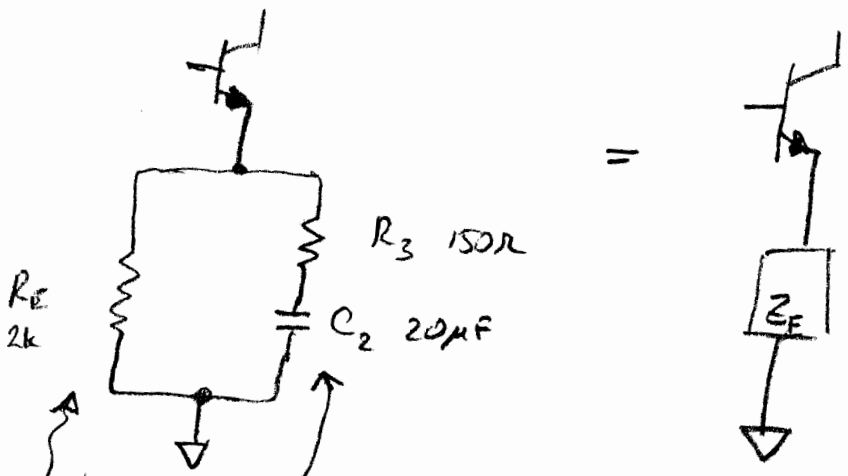

capacitor blocks dc, allows ac to pass

big emitter resistor provides stable dc (quiescent) current


this combination provides a

big ac gain
$$A_v = - \frac{R_c}{R_3 + r_e}$$

but a stable dc operation

multisim demo

Differential Amplifiers

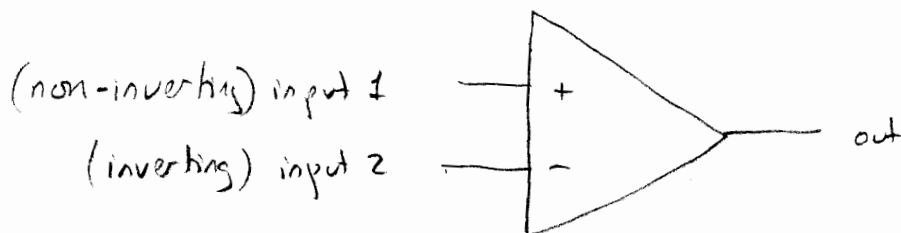


$$V_{out} = A_v^{diff} (V_{in1} - V_{in2})$$

↑ differential gain


Q. Why use a differential amp?

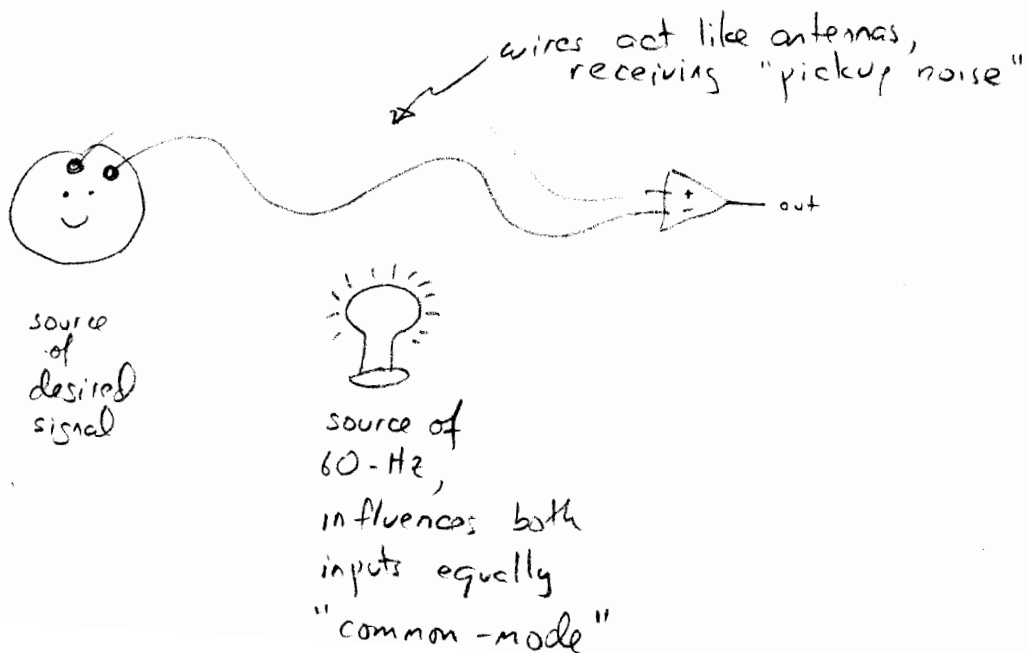A. To eliminate "common-mode noise", i.e., features in the input waveforms that are identical for both inputs



CMRR - common-mode rejection ratio

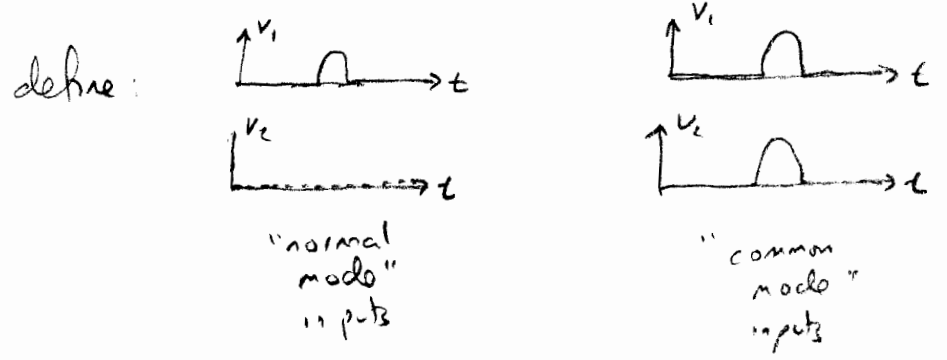
a figure of merit for how good a differential amplifier is



$$CMRR = \text{ratio} \frac{\text{amplifier output for normal mode input}}{\text{common mode input}}$$

$$= \frac{A_{\text{diff}}}{A_{\text{common}}}$$

multisim demo

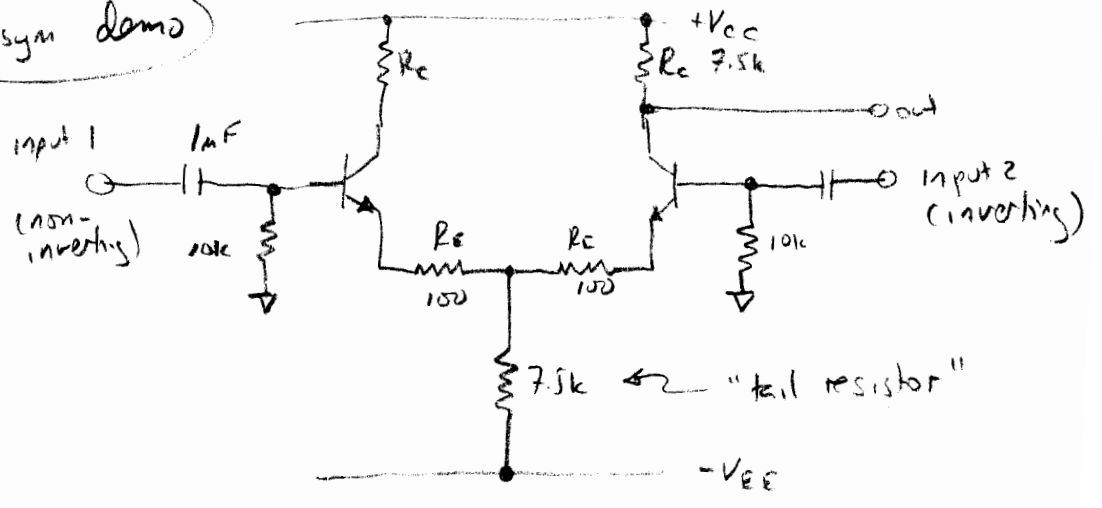

differential amplifier demo, cont.

$$\begin{aligned}
 CMRR &= \frac{\text{output for normal mode } \begin{matrix} v_i \\ \text{AA} \end{matrix} \begin{matrix} v_o \\ \text{AA} \end{matrix}}{\text{" " common mode } \begin{matrix} \text{AA} \\ \text{AA} \end{matrix} \begin{matrix} \text{AA} \\ \text{AA} \end{matrix}} \\
 &= \frac{2.72V}{0.0485V} \\
 &= 56
 \end{aligned}$$

$$20 \log_{10} 56 = 35 \text{ dB}$$

For comparison, a really good differential amp. has $CMRR = 10^6 \rightarrow 120 \text{ dB}$

Q. why isn't the common-mode gain zero?

A. $A_{\text{common}} \sim R_c/R_T$ & R_T is finite
 $A_{\text{diff}} \sim R_c/2R_E$ } see text.

show differential amplifier for biomedical use