

Electronics Lab

This document contains two sample lab reports.

The instructions that were followed by the students have since been updated, so that your report may require a few different items.

1. Scanned image of a lab report for Lab #1.

This paper was one of the best in the class in its year, although it is not as easy to read as the next example.


2. Scanned image of a lab report for Lab #2.

This is a perfect lab report for Lab #2. In addition to having perfect content, it is also very easy to read.

Laboratory Report 1

Preface: This report serves as a summary of the basic procedures the student carried out to familiarize himself with common electronic laboratory equipment, simple circuits, error analysis, and basic circuit concepts.

Section 1, part A

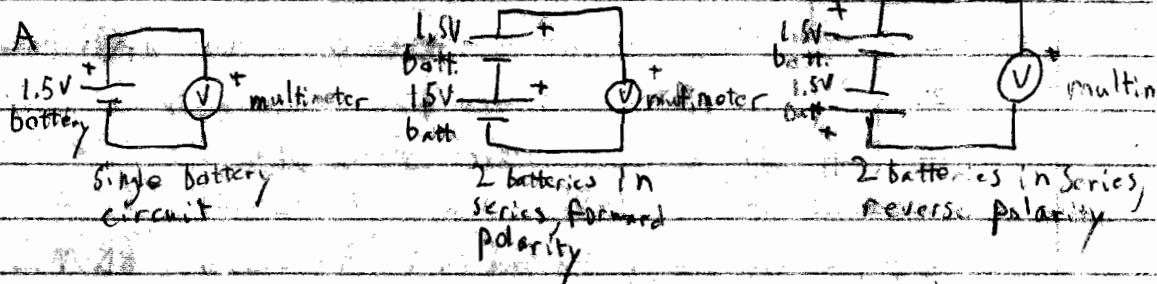

instruments used: BK Model 388-HD multimeter

Voltage across the multimeter was measured for each circuit shown. The number of batteries & their relative orientations were varied. Errors were estimated based on the specifications given in the manual (Goree, vii).

$$V_{\text{batt1}} = 1.561 \text{ V} \pm 8.8 \times 10^{-3} \text{ V}$$

$$V_{\text{batt2}} = 1.565 \text{ V} \pm 8.8 \times 10^{-3} \text{ V}$$

$$V_{\text{2F}} = 3.11 \text{ V} \pm 0.026 \text{ V}$$

$$V_{\text{2R}} = 2.047 \text{ V} \pm 1.2 \times 10^{-3} \text{ V}$$

$$V_{\text{Fetc}} = 3.126 \text{ V} \pm 1.24 \times 10^{-2} \text{ V}$$

$$V_{\text{Retc}} = 4 \times 10^{-3} \text{ V} \pm 1.24 \times 10^{-2} \text{ V}$$


prop. of errors

$$V_{\text{etc}} = V_1 \pm V_2 \Rightarrow \Delta V_{\text{etc}} = \left(\frac{\partial V_{\text{etc}}}{\partial V_1} \Delta V_1 \right)^2 + \left(\frac{\partial V_{\text{etc}}}{\partial V_2} \Delta V_2 \right)^2 = (\Delta V_1)^2 + (\Delta V_2)^2 = \Delta V_1^2 + \Delta V_2^2$$

$$\Delta V_c = \sqrt{(8.8 \times 10^{-3})^2 \cdot 2} = 1.24 \times 10^{-2} \text{ V}$$

The error ranges of V_{2F} and V_{Fetc} overlap, as do the error ranges of V_{2R} and V_{Retc} , indicating these experimental values agree with theoretical calculation.

Part B

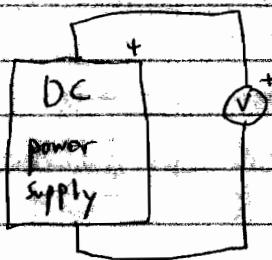

Two voltages produced by the power supply were measured. The measured voltage output by the power supply was varied. Errors were estimated as in part A (Goree, vii) for multimeter and estimated at $\pm 1 \text{ V}$ for the eye for DC power supply.

Instruments Used: BK model 388-HD multimeter $\pm 5 \text{ uV}$

HP 721 A DC supply

according to multimeter


$$V_{1m} = 50.8 \text{ V} \pm 0.354 \text{ V} \quad V_2 = 80.5 \text{ V} \pm 0.0503 \text{ V}$$

according to DC supply

$$V_1 = 50 \text{ V} \pm 1 \text{ V} \quad V_2 = 80 \text{ V} \pm 1 \text{ V}$$

The error bars for both V_1 measurements overlap, as do those for the V_2 measurements, indicating that both measurements are reasonable.

Part 2

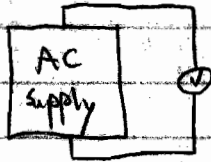

RMS voltage output and frequency of the AC source were measured. Nothing was varied. No errors were estimated.

Equipment used: Custom built AC supply, BK Model 388 HD Multimeter
 $V_{\text{ac rms}} = 8.14 \text{ V}$ (8 V expected)
 $f = 60 \text{ Hz}$ (60 Hz expected)

Part 3, part A





The resistances of 10 resistors were measured & compared to the value of resistance recorded on the resistor. Only resistance was varied. Errors were calculated as $\frac{\Delta V}{V}$ ($\Delta V_{\text{rec}}, V_{\text{ii}}$)

Instruments used: BK Model 388 HD Multimeter

Color Code	Nominal Value (Ω)	Tolerance	Measured Value (Ω)	Multimeter Scale	Mult error	error fraction
* Yel Blu Org Sil	46×10^3	10%	48.8×10^3	200K	± 466	0.00954
* Grn Red Org Sil	82×10^3	10%	85.7×10^3	200K	± 743	0.00897
* Grn Blu Red Sil	56×10^2	10%	57.3×10^2	20K	± 53	0.0093
Grn Blk Yel Sil	50×10^4	10%	55.8×10^4	2M	± 5185	0.00929
* Brn Red Red Gol	12×10^2	5%	12.74×10^3	2K	± 10.6	0.00832
Brn Blu Red Gol	16×10^2	5%	11.799×10^3	2K	± 14.5	0.00806
Grn Brn Blk Gol	51×10^0	5%	54.1	200	± 0.506	0.00935
Brn Grn Blk Gol	15×10^0	5%	18.8	200	± 0.241	0.0128
* Brn Grn Org Gol	15×10^3	5%	14.34×10^3	20K	± 118	0.00823
* Brn Red Org Sil	12×10^3	10%	12.49×10^3	20K	± 104	0.00833

* falls within specified tolerance

Part B

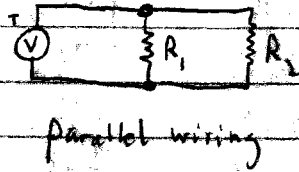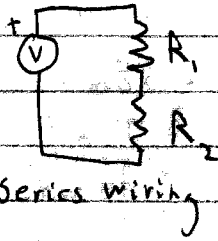

The resistance across the shown circuit setup was measured. Only circuit layout was varied. Errors were calculated as before in la (Goree, vii).

Equipment used: BK Model 388HD Multimeter

$$R = 48.8 \times 10^3 \Omega \pm 466 \Omega$$

$$R_{\text{series (m)}} = 63.1 \times 10^3 \Omega \pm 570 \Omega$$

$$R_2 = 14.34 \times 10^3 \Omega \pm 118 \Omega$$

$$R_{\text{par (m)}} = 11.0 \times 10^3 \Omega \pm 180 \Omega$$

$$R_{\text{series (calc)}} = R_1 + R_2 = 63.14 \times 10^3 \Omega \pm 570 \Omega$$

$$\Delta R^2 = (\Delta R_1)^2 + (\Delta R_2)^2 = (466 \Omega)^2 + (118 \Omega)^2 = (570 \Omega)^2$$

$$R_{\text{parallel (calc)}} = (R_1^{-1} + R_2^{-1})^{-1} = 11.08 \times 10^3 \Omega \pm 240 \Omega$$


$$\Delta R^2 = \left(\frac{dR}{dR_1} \Delta R_1\right)^2 + \left(\frac{dR}{dR_2} \Delta R_2\right)^2$$

$$dR = -(R_1^{-1} + R_2^{-1})^{-2} \cdot -1 R_1^{-2} = \frac{1}{(R_1^{-1} + R_2^{-1}) R_1^2}$$

$$\Delta R = \sqrt{(4.65 \times 10^{-5} \cdot 48.8 \times 10^3)^2 + (5.39 \times 10^{-5} \cdot 14.34 \times 10^3)^2} \text{ of } R$$

$$\frac{dR}{dR_1} = \frac{1}{(R_1^{-1} + R_2^{-1}) R_1^2} = 5.39 \times 10^{-5} \text{ } \Omega^{-1}$$

$$\Delta R = 290 \Omega$$

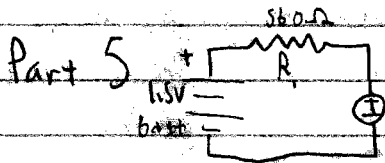

The value of R was measured, and then current was measured directly through the circuit as well as being calculated. Nothing was varied. Errors were measured as in la (Goree, vii)


Instruments Used: BK Model 388 HD Multimeter

$$R_{\text{m}} = 559 \Omega \pm 5.19 \Omega$$

$$I_{\text{m}} = 2.7 \text{ mA} \pm 0.127 \text{ mA}$$

$$\frac{V}{R} = I_{\text{calc}} = 2.68 \text{ mA}$$

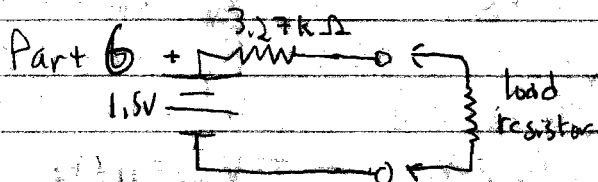This calculated value is within the error bars of the measured value for I , indicating experimental value matches prediction, as well as current in circuit.



Voltage across load was measured. Load Resistance was varied. Error was calculated as in la (Goree, vii).


Instruments used: BK Model 388 HD Multimeter, General Radio Co. 1432-S Decade Resistor

load Resistor (k Ω)	Current	Voltage across load
0.3	0.421mA \pm 0.00521mA	132mV \pm 1.66mV
0.7	0.380mA \pm 0.00480mA	276mV \pm 2.38mV
1.5	0.318mA \pm 0.00418mA	491mV \pm 3.46mV
3	0.243mA \pm 0.00343mA	748mV \pm 4.74mV
4.5	0.197mA \pm 0.00297mA	906mV \pm 5.53mV
6	0.166mA \pm 0.00266mA	1013mV \pm 6.065mV


a. In this case, measuring current will be more accurate, since measuring voltage & calculating current flow will result in the propagation of errors, since resistance also has an error value associated with it. It's actually not that trivial.

b. please see attached graph.

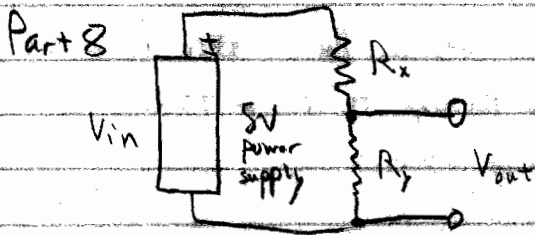c. $I_{load} = \frac{V}{R} = \frac{1.5V}{3.27 \times 10^3 \Omega} = 0.459mA \times 90\% = 0.413mA$ (from graph, 90% cutoff \approx 0.9k Ω)



unloaded voltage divider

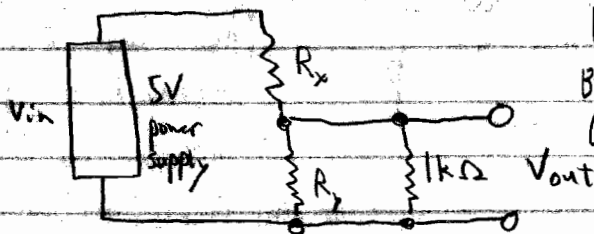

loaded voltage divider

Instruments Used

- Heathkit 5V power supply
- BK Model 388 HD Multimeter
- General Radio Co. 1932-S Decade Resistor

Input & Output Voltage were measured for the above circuits. The resistances R_x & R_y were varied. No errors were calculated.


unloaded		loaded	
$R_x = 3.27k\Omega$	$R_x = 1.60k\Omega$	$R_x = 3.27k\Omega$	$R_x = 1.60k\Omega$
$R_y = 1.60k\Omega$	$R_y = 3.27k\Omega$	$R_y = 1.60k\Omega$	$R_y = 3.27k\Omega$
$V_{in} = 4.92V$	$V_{in} = 4.96V$	$V_{in} = 4.92V$	$V_{in} = 4.96V$
$V_{out} = 3.34V$	$V_{out} = 1.634V$	$V_{out} = 0.788V$	$V_{out} = 1.824V$
$V_{out}/V_{in} = 0.679$	$V_{out}/V_{in} = 0.329$	$\frac{V_{out}}{V_{out(unloaded)}} = 48.8\%$	$\frac{V_{out}}{V_{out(unloaded)}} = 48.8\%$
$V_{out}/V_{in} (calc) = \frac{R_x}{R_x + R_y} = \frac{3.27k\Omega}{4.87k\Omega}$	$V_{out}/V_{in} (calc) = 0.328$	theoretical value of above ratio: 5=	theoretical value of above ratio:
$\epsilon = 0.671$			

Both experimental values are within 2 sig figs of the calculated values.

back of attached graph (#1)

see back of attached graph (#2)

Current at Various Load Resistances

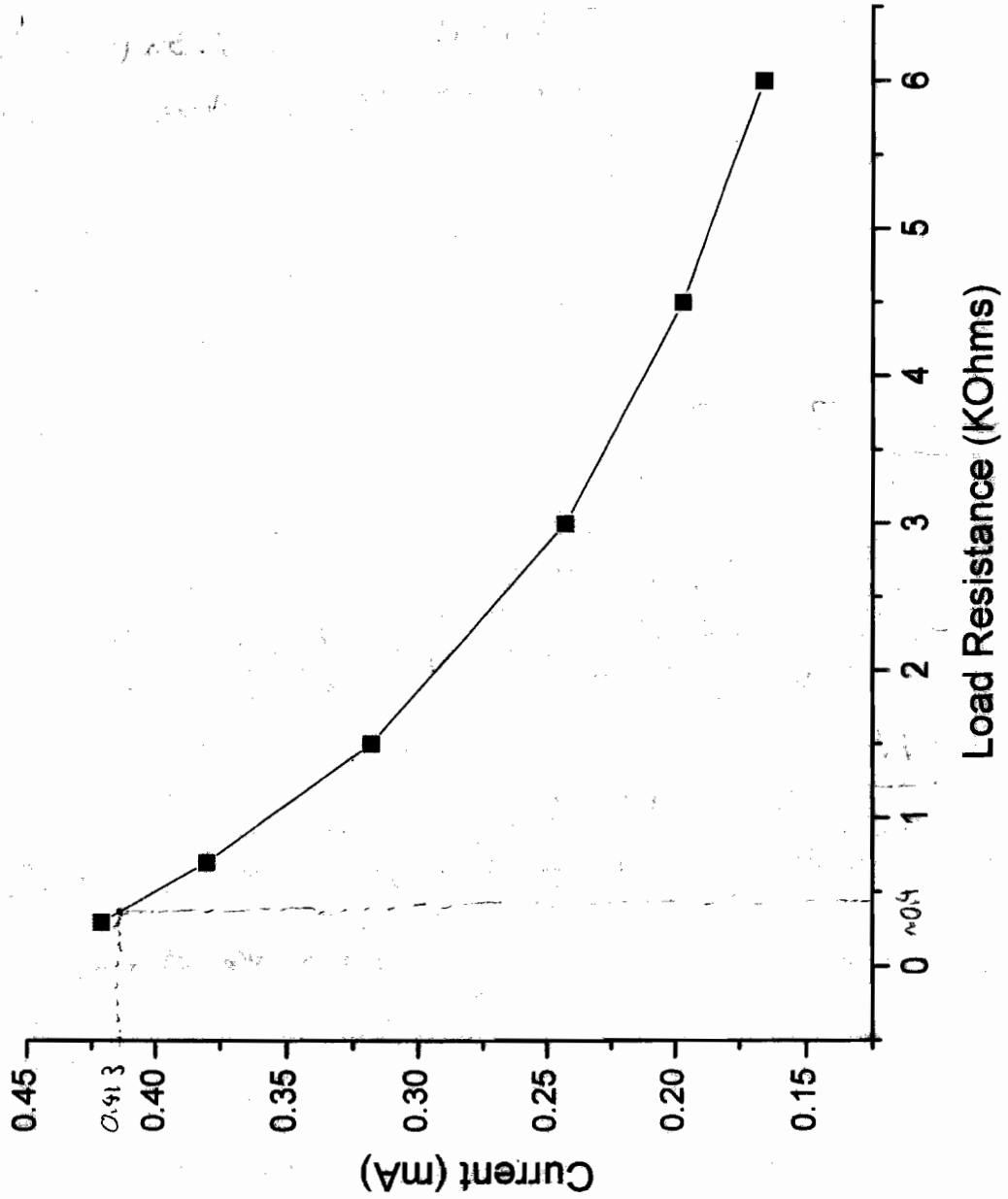

$$R_{eq} = \frac{1}{\frac{1}{R_y} + 1 \times 10^{-3}} = 615 \Omega$$

$$\frac{V_{out}}{V_{in}} = \frac{R_{eq}}{R_x + R_{eq}} \rightarrow V_{out} = \frac{R_{eq} V_{in}}{R_x + R_{eq}} = \frac{615 \Omega \cdot 4.92 V}{(615 + 3270) \Omega} = 0.779 V$$

$$\frac{0.779 V}{1.03 V} \times 100\% = 47.7\%$$

↳ This value is comparable to the experimental ratio, suggesting that the calculation + measurement reinforce one another. (48.2%)

$$2. R_{eq} = \frac{1}{\frac{1}{3.27 k\Omega} + \frac{1}{1000 \Omega}} = 766 \Omega$$

$$V_{out} = \frac{R_{eq} V_{in}}{R_x + R_{eq}} = \frac{766 \Omega \cdot 4.96 V}{(766 \Omega + 1660 \Omega)} = 1.57 V$$

$$\frac{1.57 V}{3.34 V} \times 100\% = 47.0\%$$

↳ this value is comparable to the experimental ratio, suggesting that the calc + measurement reinforce one another. (48.6%)

Electronics Lab

This is a sample lab report for Lab #2.

The instructions that were followed by the student here have since been updated, so that your report may require a few different items.

Lab 2: AC Measurement

100

Preface

- Measure AC signal (amplitude, frequency, phase) using oscilloscope
- Study AC circuits


Experiment

1. Measurement of Voltages

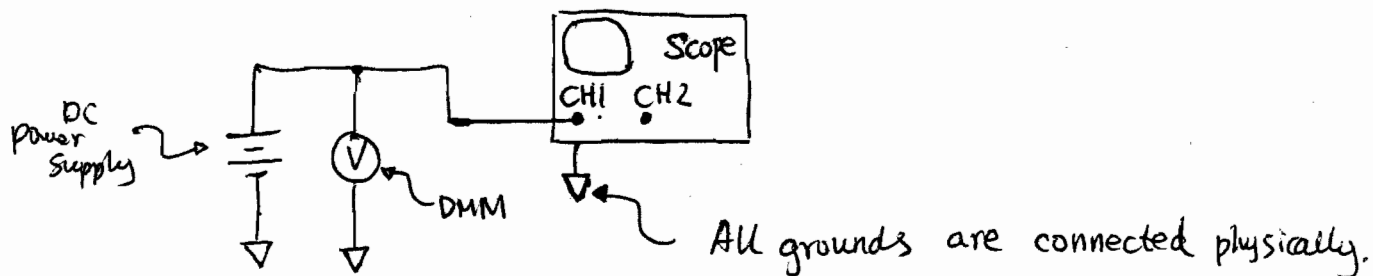(a) DC voltage

Apparatus: oscilloscope, digital multimeter, power supply

Procedure: set up scope;
set output voltage of power supply;
measure the output voltage using the scope & the multimeter.



Voltage set by power supply	voltage measured by multimeter	scale of multimeter	voltage measured by scope	scale of scope
$(1 \pm 0.25) V$	$(1.252 \pm 0.007) V$	4V	$(1.25 \pm 0.05) V$	$0.5 V/Div$
$(2 \pm 0.25) V$	$(2.322 \pm 0.013) V$	4V	$(2.35 \pm 0.05) V$	$0.5 V/Div$
$(3 \pm 0.25) V$	$(3.260 \pm 0.017) V$	4V	$(3.30 \pm 0.05) V$	$0.5 V/Div$


↙ Half the minimum scale, i.e. $\frac{1}{2} \times 0.5V$
 ↘ according to DMM's specification
 ↘ Half minimum division multiplied by scale, i.e. $0.1 \text{ div} \times 0.5V/Div$

The meter is more precise than oscilloscope, although the precision of oscilloscope's measurement can be improved by choosing smaller scale for vertical display.

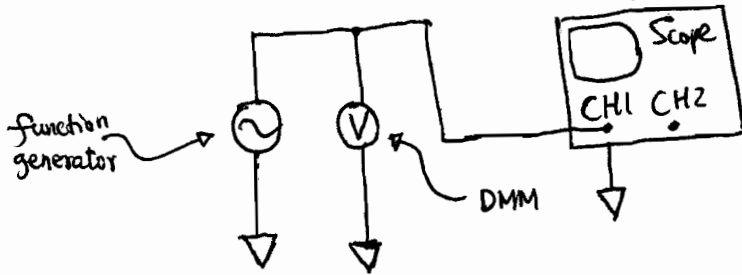(b) AC Voltages

Apparatus: oscilloscope, digital multimeter, function generator

procedure: connect circuit;
set up function generator;
measure RMS voltage using multimeter & peak-to-peak voltage using scope.



Results:

$$V_{\text{RMS}} = (342.4 \pm 1.8) \text{ mV} \quad \left(\frac{\delta V}{V} \right)_{\text{DMM}} = 0.5\%$$

By DMM
400 mV scale

$$V_{\text{peak-to-peak}} = (1.00 \pm 0.02) \text{ V}$$

by scope
0.2 V/div


$\div 2\sqrt{2}$ $\div 2\sqrt{2}$

$$V_{\text{RMS}} = (0.35 \pm 0.01) \text{ V} \quad \left(\frac{\delta V}{V} \right)_{\text{scope}} = 2.9\%$$

calculated using
 $V_{\text{peak-to-peak}}$

The meter is more precise, as seen from $\left(\frac{\delta V}{V} \right)_{\text{scope}} > \left(\frac{\delta V}{V} \right)_{\text{DMM}}$

(c) AC & DC coupling

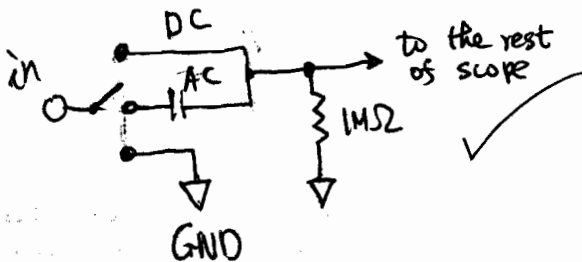

Difference: using DC coupling, one can see a vertical deflection of the trace when changing the offset; for AC coupling, there is no response to DC offset.

When using AC coupling, the signal passes a capacitor, which blocks the DC offset.

2. Measurement of Frequency

Apparatus: oscilloscope, digital multimeter, function generator

procedure: prepare the circuit as in (b) & (c);
measure frequency using multimeter;
measure time per cycle using scope & calculate frequency.

Frequency by
multimeter

10.25 kHz

uncertainty in
DMM measurement

0.13 kHz

Frequency
by scope

10309 Hz
(using 10 μs/Div)

uncertainty in
scope measurement

103 Hz

using $\left| \frac{\delta f}{f} \right| = \left| \frac{\delta T}{T} \right|$

15% = $\left| \frac{\delta T}{T} \right|$


frequency

period

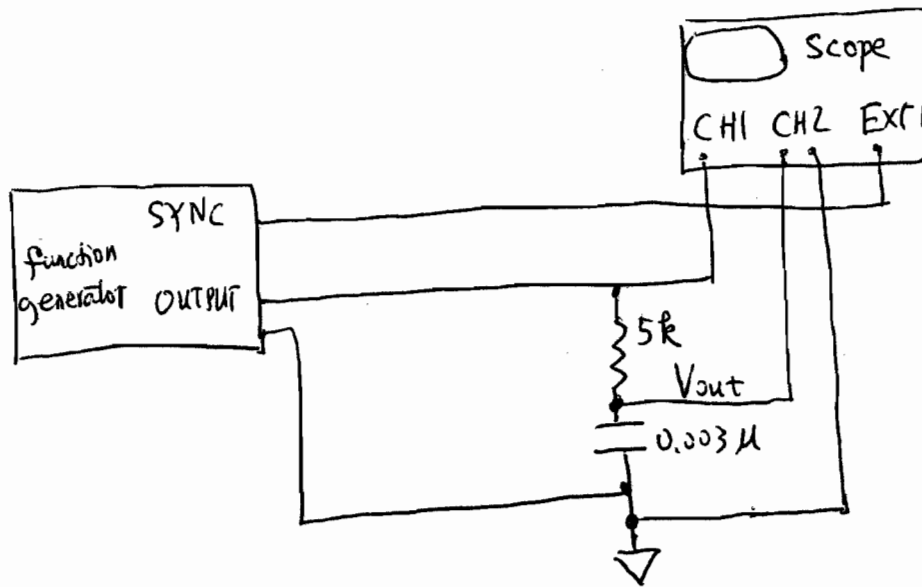3. Time constant of an R-C circuit

Apparatus: Oscilloscope, digital multimeter, function generator, $5\text{ k}\Omega$ resistor, $0.003\text{ }\mu\text{F}$ capacitor

Procedure: Connect circuit
set function generator & the scope
measure charging & discharging times



Results:


$$R = 5.60\text{ k}\Omega \pm 0.04\text{ k}\Omega$$

$$C = 3.50\text{ nF} \pm 0.11\text{ nF}$$

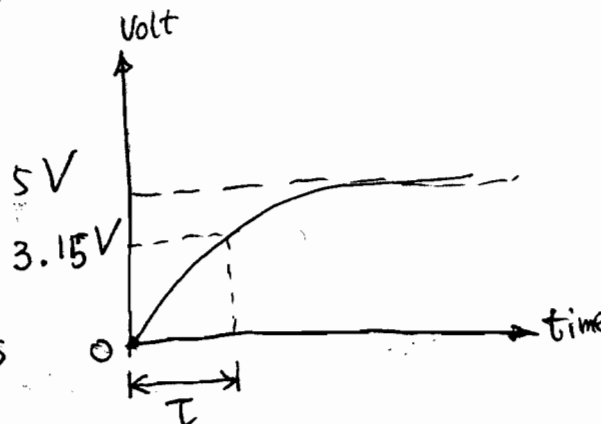(a) Charging time

$$\begin{aligned} \text{charge } T_{\text{measure}} &= (2.0 \pm 0.1) \times 10^{-2} \text{ ms} \\ \text{by scope } & \\ 10\text{ }\mu\text{s}/\text{Div} & \\ &= 20.0\text{ }\mu\text{s} \pm 1.0\text{ }\mu\text{s} \end{aligned}$$

$$\frac{\text{charge } T_{\text{measure}}}{RC} = 1.02$$




(b) Discharging time


$$T_{\text{measure}}^{\text{discharge}} = (1.85 \pm 0.1) \times 10 \mu\text{s}/\text{Div}$$

$$= 18.5 \mu\text{s} \pm 1.0 \mu\text{s}$$
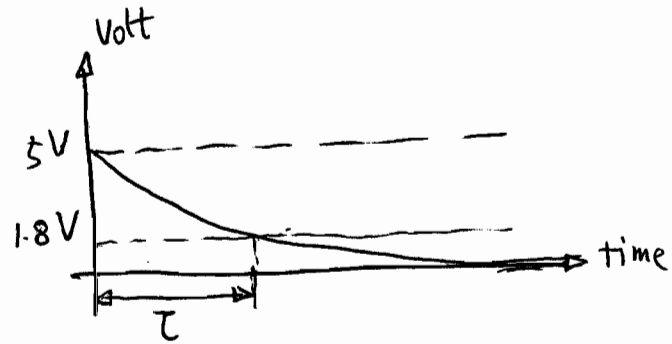
$$\frac{T_{\text{measure}}^{\text{discharge}}}{RC} = 0.94$$



4. R-C Low-Pass Filter

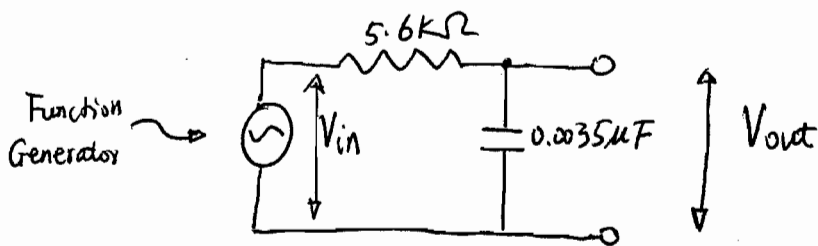

Apparatus: same as 3

Procedure:

- connect circuit as in 3
- set function generator & scope
- measure V_{out} & V_{in} at various frequencies.
- measure time delay τ between V_{out} & V_{in} .

Results:

(a) Amplitude response


- (i) see next page.
- (ii) see next page.
- (iii) The frequency at $\frac{V_{\text{out}}}{V_{\text{in}}} = 0.707$ is

$f_{\text{measure}} = (8.32 \pm 0.11) \text{ kHz}$	}	$\Rightarrow \frac{f_{\text{measure}}}{f_{\text{calculated}}} = 1.02$
$f_{\text{calculated}} = \frac{1}{RC} = 8.12 \text{ kHz}$		

$R = 5.60 \text{ k}\Omega \pm 0.04 \text{ k}\Omega$
 $C = 3.50 \text{ nF} \pm 0.11 \text{ nF}$

f (Hz)	δf	V_{in}	δV_{in}	V_{out}	δV_{out}	V_{out}/V_{in} (measure)	V_{out}/V_{in} (theory)
0.011	0.001	4.8	0.1	4.8	0.1	1.0	1.00
0.021	0.001	4.9	0.1	4.6	0.1	0.9	1.00
0.05	0.002	4.8	0.1	5.0	0.2	1.0	1.00
0.1	0.002	5.0	0.1	5.0	0.2	1.0	1.00
0.201	0.003	5.0	0.1	5.0	0.2	1.0	1.00
0.501	0.006	5.1	0.1	5.0	0.2	1.0	1.00
1.001	0.011	5.1	0.1	4.9	0.1	1.0	0.99
1.999	0.021	5.1	0.1	4.9	0.1	1.0	0.97
5.02	0.06	5.0	0.1	4.3	0.1	0.9	0.85
10.09	0.11	5.1	0.1	3.2	0.1	0.6	0.63
20.7	0.3	5.1	0.1	1.95	0.02	0.4	0.37
50.8	0.6	5.0	0.1	0.82	0.02	0.2	0.16
100.1	1.1	5.1	0.1	0.44	0.02	0.1	0.08
200.1	2.1	5.1	0.1	0.22	0.01	0.0	0.04
500.0	5.1	5.0	0.1	0.086	0.002	0.0	0.02

$\delta A =$ uncertainty in A
Spelling

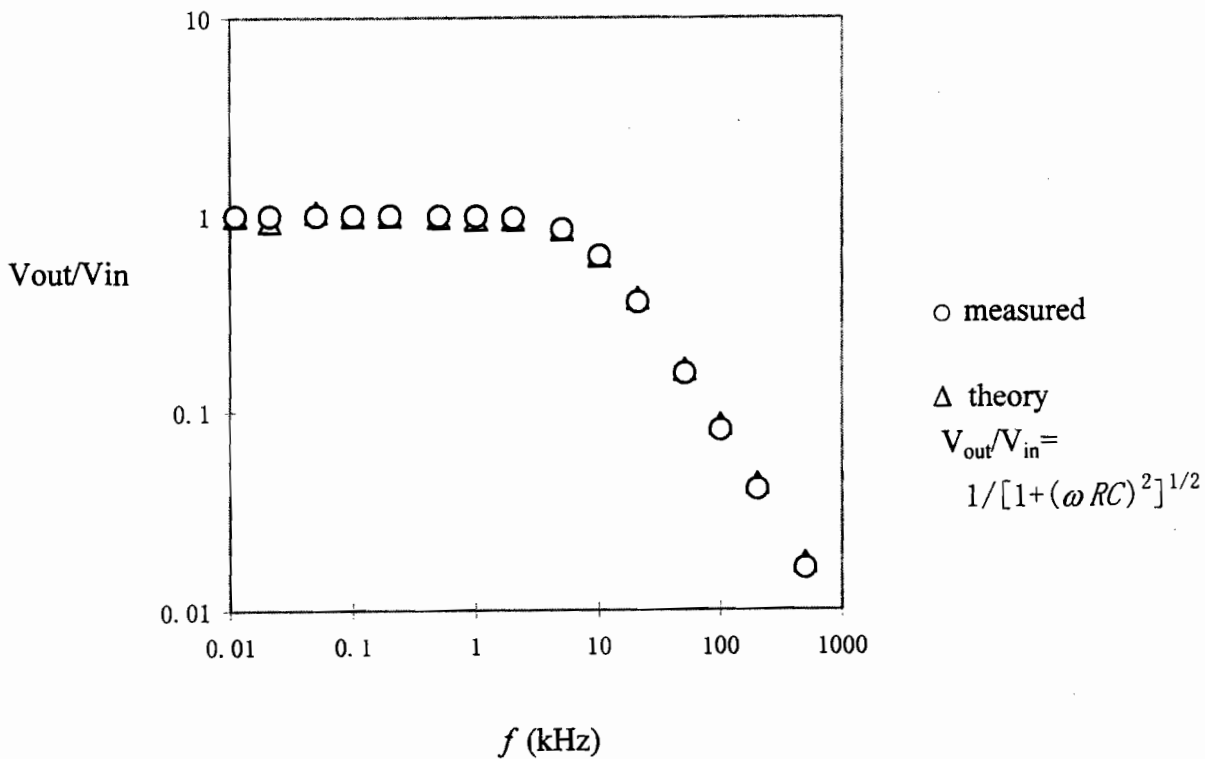

Amplitude Response of A Low-Pass Filter

(b) Phase Response

(i) see next page

(ii) see next page

(iii) The phase angle at $f = \frac{1}{2\pi RC}$:

$$f = 8.1 \text{ kHz}$$

$$\theta_{\text{measure}} = 43.15^\circ \pm 0.93^\circ$$


$$\theta_{\text{theory}} = \arctan \omega RC$$

$$= \arctan (2\pi f \cdot RC)$$

$$= 45^\circ$$


R= 5.60 kΩ ± 0.04 kΩ
 C= 3.50 nF ± 0.11 nF

f (kHz)	δf (kHz)	delay in msec (τ)	$\delta\tau$ msec	phase in degrees θ (measure)	$\delta\theta$ degree	phase in degrees (theory)
0.011	0.003	0.0000	0.0001	0.000	0.000	0.078
0.021	0.003	0.0000	0.0001	0.000	0.000	0.148
0.049	0.003	0.030	0.005	0.529	0.096	0.346
0.108	0.004	0.020	0.005	0.778	0.197	0.762
0.204	0.005	0.018	0.002	1.322	0.150	1.439
0.502	0.008	0.018	0.001	3.253	0.188	3.538
1.001	0.013	0.0180	0.0005	6.486	0.199	7.028
1.962	0.023	0.0180	0.0005	12.714	0.382	13.584
5.08	0.08	0.0165	0.0005	30.18	1.03	32.033
10.26	0.13	0.0134	0.0002	49.49	0.98	51.653
20.01	0.23	0.0090	0.0002	64.83	1.62	67.937
50.1	0.8	0.0043	0.0001	77.6	2.2	80.830
100.1	1.3	0.00225	0.00005	81.1	2.1	85.403
202.0	2.3	0.00144	0.00002	104.7	1.9	87.741
509.0	5.4	0.00049	0.00001	89.8	2.1	89.131

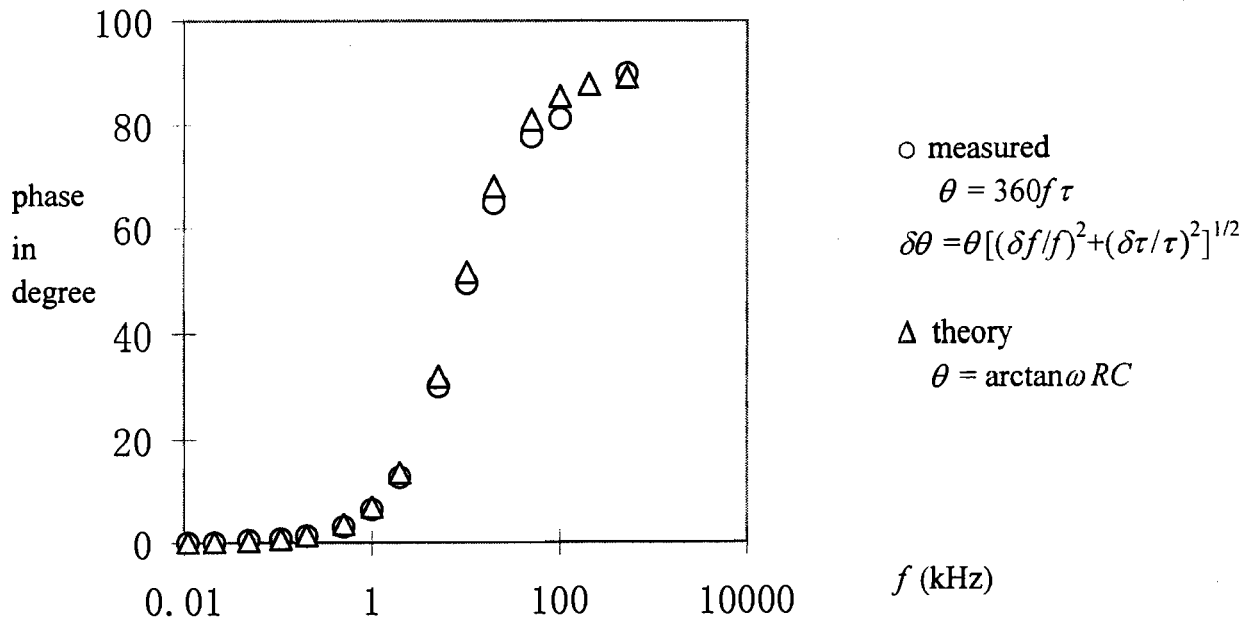

Phase Response of A Low-Pass Filter

5. R-C High-Pass Filter

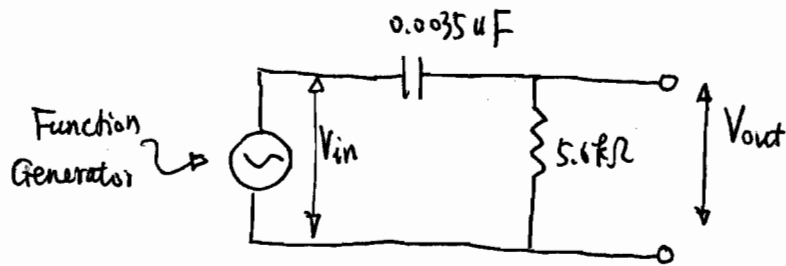

Apparatus : same as 3

Procedure :

connect circuit as above;

set function generator & scope

measure V_{out} & V_{in} at various frequencies

Results :


(i) See data table in the next page;

(ii) Amplitude response in the next page.

$R = 5.60 \text{ k}\Omega \pm 0.04 \text{ k}\Omega$
 $C = 3.50 \text{ nF} \pm 0.11 \text{ nF}$

f (kHz)	δf	V_{in}	δV_{in}	V_{out}	δV_{out}	V_{out}/V_{in} (measure)	V_{out}/V_{in} (theory)
0.012	0.003	5.0	0.1	0.000	0.001	0.0	0.00
0.022	0.003	5.0	0.1	0.000	0.001	0.0	0.00
0.051	0.004	5.0	0.1	0.028	0.001	0.0	0.01
0.103	0.004	4.9	0.1	0.057	0.001	0.0	0.01
0.201	0.005	5.0	0.1	0.100	0.001	0.0	0.02
0.498	0.008	4.8	0.1	0.333	0.002	0.1	0.06
1.065	0.014	4.9	0.1	0.559	0.005	0.1	0.13
2.207	0.025	5.0	0.1	1.05	0.02	0.2	0.26
5.16	0.08	5.0	0.1	2.33	0.02	0.5	0.54
10.03	0.13	4.9	0.1	3.5	0.1	0.7	0.78
20.65	0.24	5.0	0.1	4.3	0.1	0.9	0.93
50.1	0.6	5.0	0.1	4.6	0.1	0.9	0.99

$\delta A = \text{uncertainty in } A;$

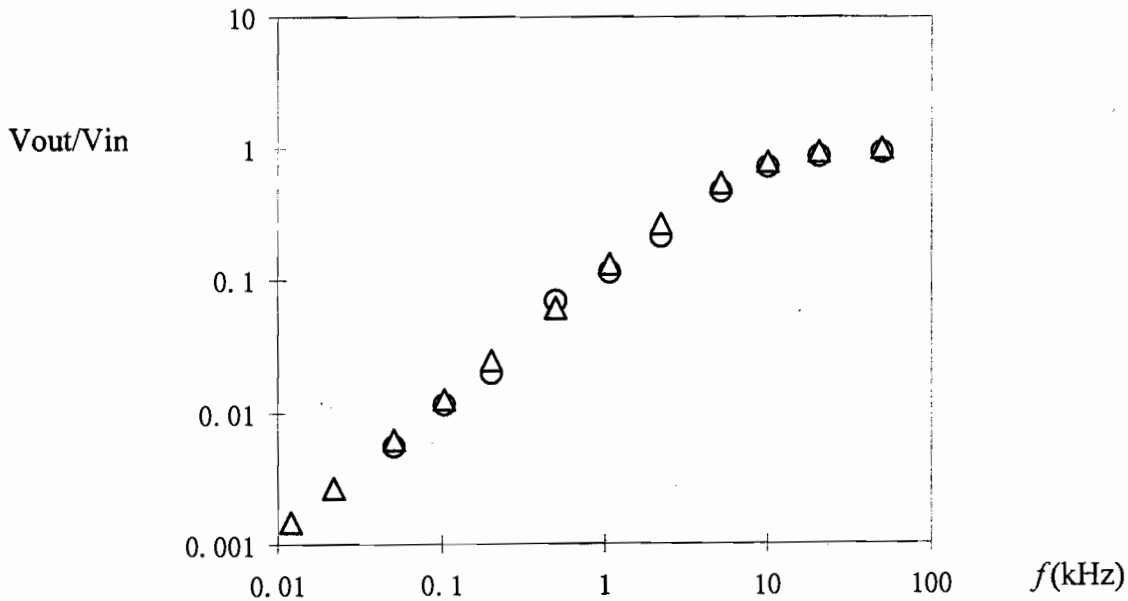

○ measured

△ theory

$$V_{out}/V_{in} = \omega RC / [1 + (\omega RC)^2]^{1/2}$$

High-Pass filter