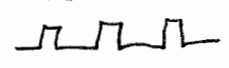


Chap. 5 Oscillators


Oscillators are part of most instruments.

Oral discussion:


- signal generators
 - function "
 - pulse "
- } obviously include an oscillator
-
- digital instruments
 - computers
 - anything with a display that refreshes periodically
- } requires a clock 
-
- time measurement
 - freq counter, counts events between a start & stop time ← clock
-
- analog oscilloscope
 - to sweep e-beam horizontally across screen



kinds of oscillators

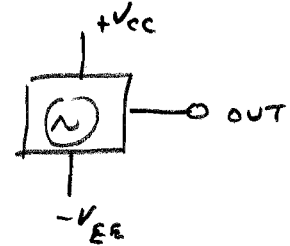all have an output

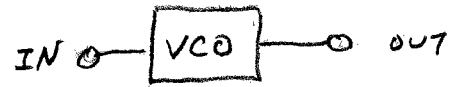


some have an input



FM freq modulation 
 AM amplitude modulation 

positive feedback

Oscillators use positive feedback

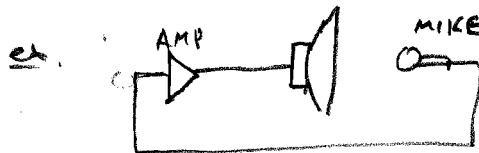

timing methods



- quartz crystal
 - it's an LCR resonant circuit in a single package
 - 0.01% or better accuracy
- RC relaxation oscillators
 - period determined by product RC
 - not as accurate, but easier, than quartz crystal. ← student projects!

recall

RC time



charge $Q = C V$
 ↑
 potl. across capacitor

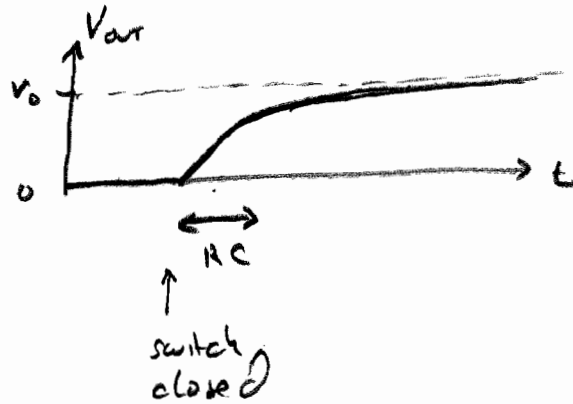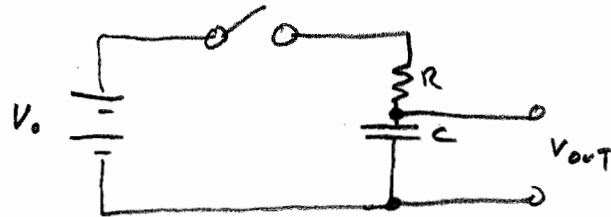charging starts when switch below is closed




discharging

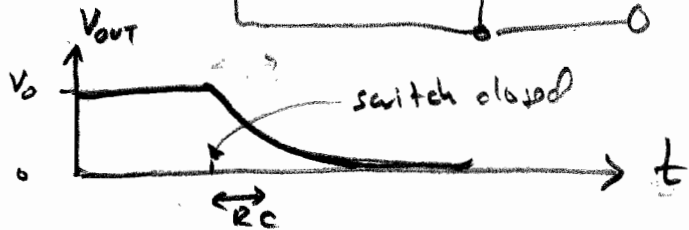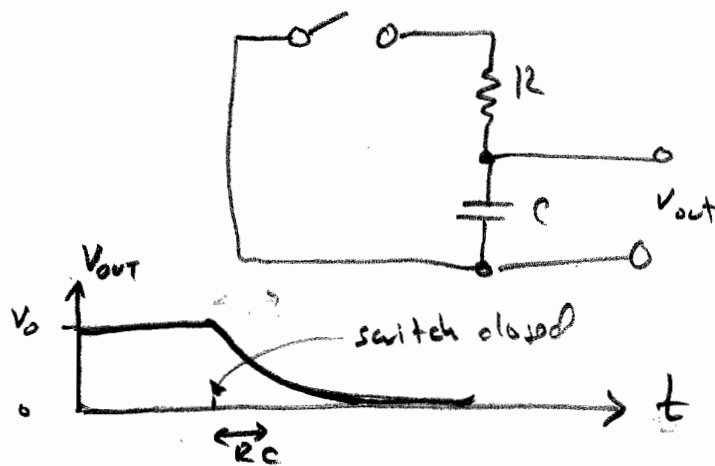if capacitor is already charged, so that initially it has a potl V_0 , then switch below is closed




555 Timer Chip

Easiest way to make a pulse train

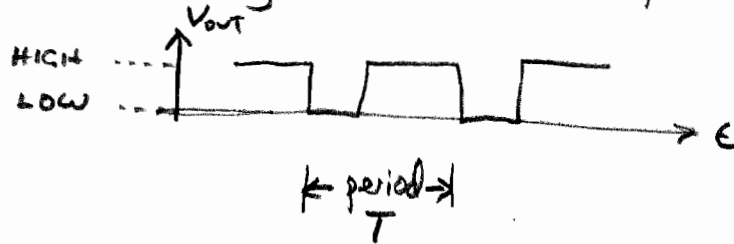

It is an 8-pin IC

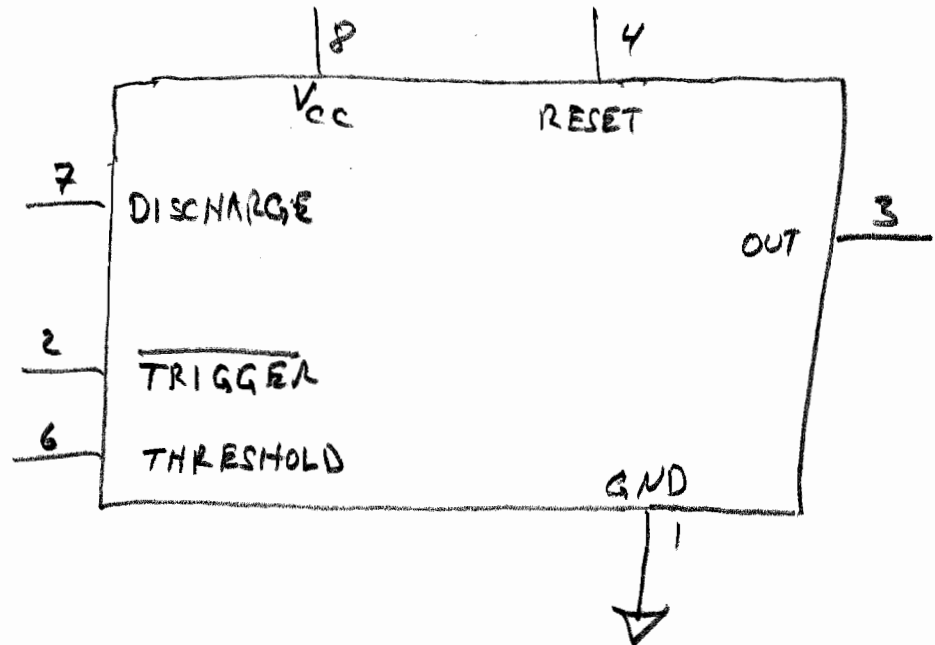

Requires a single-sided power supply

e.g. $V_{cc} = +5V$ or $+9V$
& $GND = 0V$

oral discussion: "single-sided" vs.
"dual"
power supply
op amps, digital chips, etc.

555 inputs:

pin 6 THRESHOLD is actuated by input $< \frac{1}{3}V_{cc}$

pin 2 TRIGGER " " " " " " $> \frac{2}{3}V_{cc}$

555 outputs:

pin 3 OUT a voltage, either HIGH or LOW

pin 7 DISCHARGE a transistor switch, inside the chip, determines whether pin 7 is:

- open circuit, or
- shorted to GND

555 rules

two different
input conditions

what happens at outputs

(a) $V_{\text{TRIGGER}} < \frac{1}{3}V_{cc}$

OUT \rightarrow HIGH

and

DISCHARGE pin is open

(b) $V_{\text{THRESHOLD}} > \frac{2}{3}V_{cc}$


OUT \rightarrow LOW

and

DISCHARGE pin is shorted to GND

Fig 5.33 of text:

draw
big

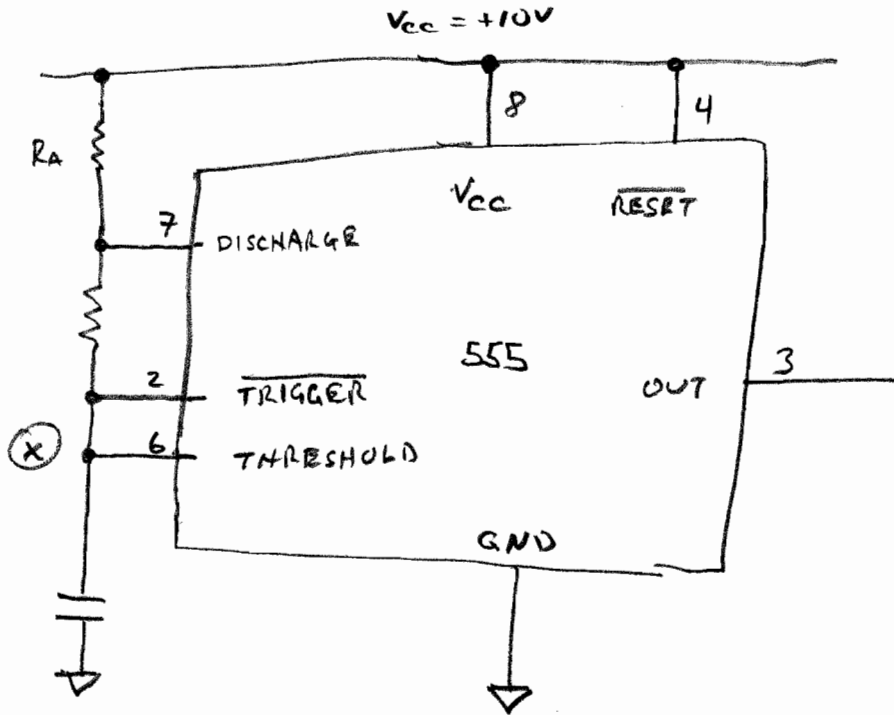

Time History, in three steps:

- ① Suppose initially C has no charge
Recall $Q = CV$
↑ volt drop across cap.

$$\Rightarrow (V_x - 0) = 0$$


node X is connected to $\overline{\text{TRIGGER}}$

$$\Rightarrow V_{\overline{\text{TRIGGER}}} = 0 < \frac{1}{3} V_{cc}$$

\Rightarrow rule ② applies

$\Rightarrow \begin{cases} \text{OUT is HIGH} \\ \text{DISCHARGE (pin 7) is open} \end{cases}$

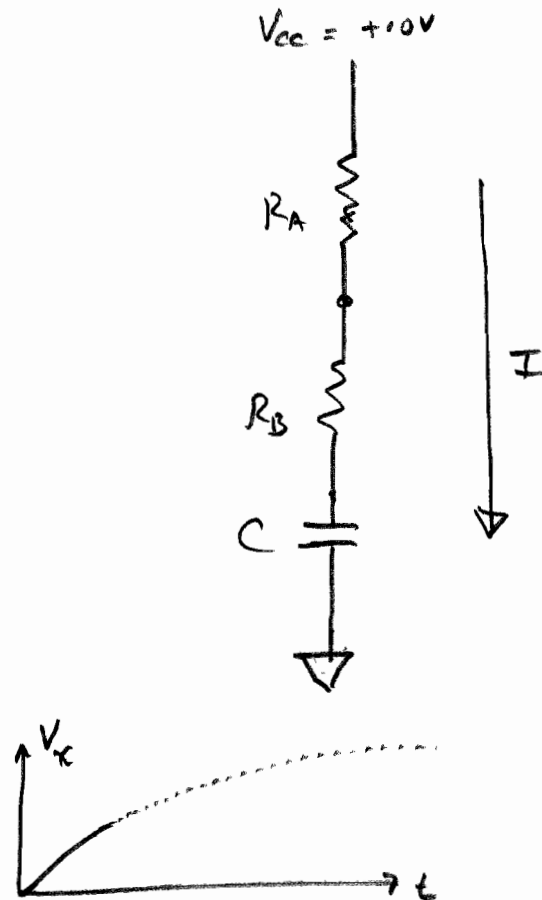so the capacitor can charge
thru R_A & R_B





② capacitor continues to charge up in step ① until

$$V_x = V_{\text{THRESHOLD}} > \frac{2}{3}V_{CC}$$

⇒ rule ⑥ applies

⇒ $\begin{cases} \text{OUT is LOW} \\ \text{DISCHARGE (pin 7) is shorted to GND} \end{cases}$

so the capacitor will discharge thru R_B

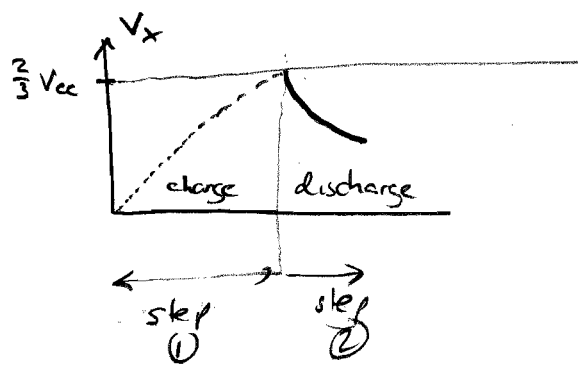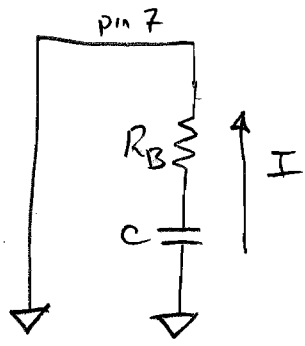

③ capacitor continue to discharge in step ② until




$$V_x = V_{\text{TRIGGER}} < \frac{1}{3} V_{cc}$$

⇒ rule @ applies again

⇒ $\left\{ \begin{array}{l} \text{OUT is HIGH} \\ \text{DISCHARGE (pin 7) is open} \end{array} \right.$

capacitor charges thru R_A & R_B

complete time history

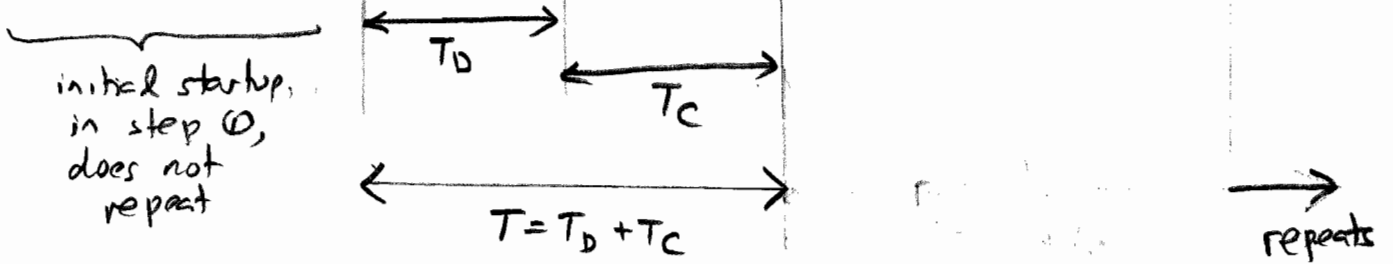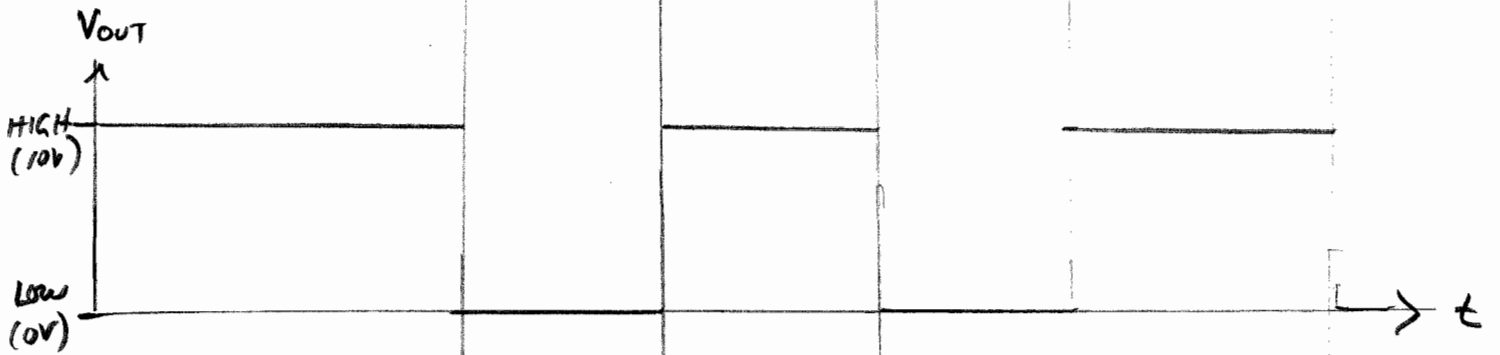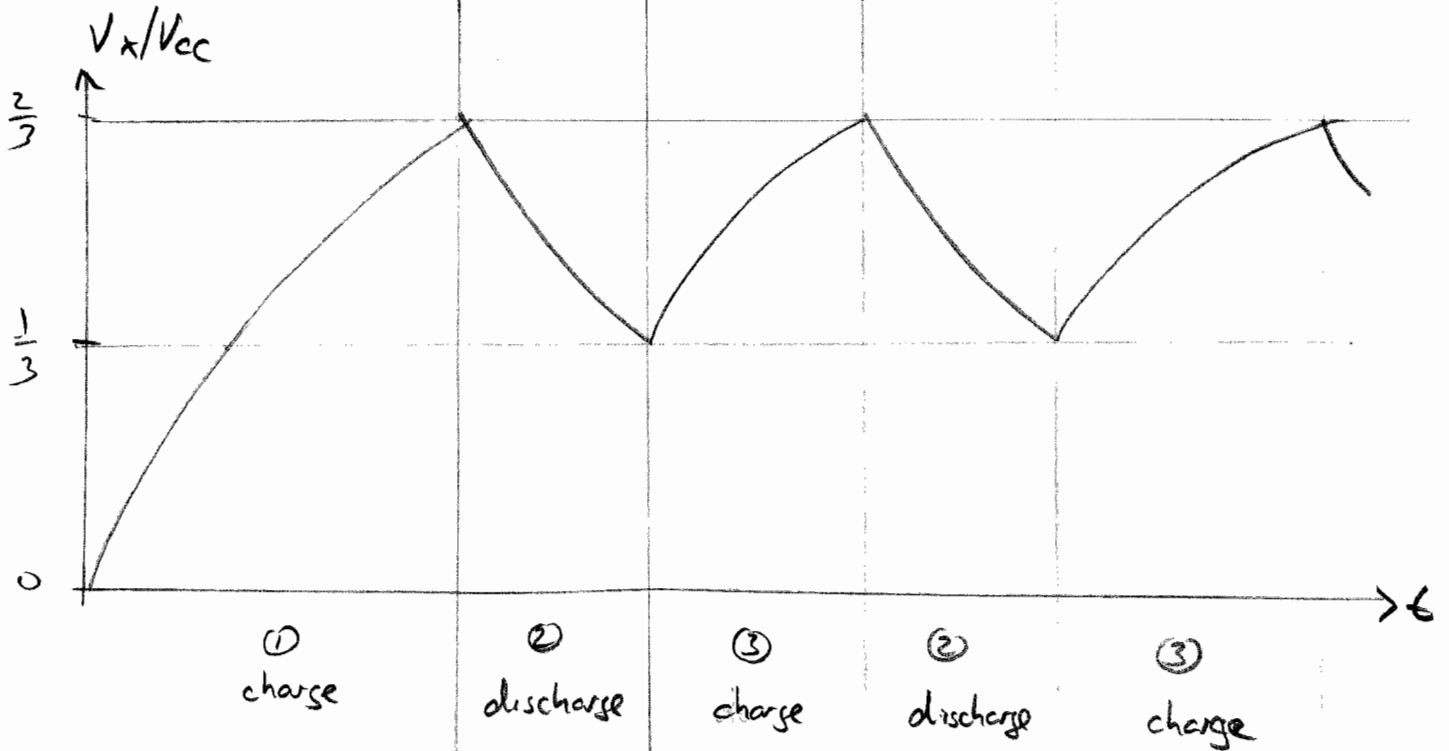

↑ period T
calculate T in homework