

Horowitz & Hill Chap. 8 Digital Electronics

"States"

HIGH ↔ TRUE ↔ 1
LOW ↔ FALSE ↔ 0

A state can be indicated by a symbol, e.g. Q


negation:

Q	\bar{Q}
0	1
1	0

sometimes written as Q'

this diagram is called a "truth table"

LEDs are often used to indicate state

 

always use a current-limiting resistor
typ. 150-330Ω

Families of digital logic

	TTL (74LSXX)	CMOS (74CXX)	High-Speed CMOS (74HCXX)
Speed	Fastest	Slowest	Almost as fast as TTL
Power Consumed	Most	Least (Best for battery-powered circuits)	
True Voltage	$T \approx +3.4V$	$T \approx +4.9V$	
False Voltage	$F \approx +0.2V$	$F \approx +0.1V$	
Power Supply	$V_{CC} = +5V$	$+5V < V_{DD} < +15V$ (9V battery is okay)	$2V < V_{DD} < 6V$

For all 3 families, the most common power-supply voltage is +5V & GND

Logic Gates

8-3

Name Symbol Boolean Truth Table

Inverter



$$Q = \bar{A}$$

A	Q
0	1
1	0

OR



$$Q = A + B$$

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

AND



$$Q = A \cdot B$$


A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

NOR



$$Q = \overline{A + B}$$

A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0

 

$$Q = \overline{A \cdot B}$$


A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0



$$Q = A \oplus B$$

↑ "exclusive or"

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

 

$$Q = A$$


A	Q
0	0
1	1

Boolean Math

you can work problems by making a big truth table:

inputs → intermediate steps → output

ex $Q = \bar{A} \cdot \bar{B}$

 

inputs				output
A	B	\bar{A}	\bar{B}	Q
0	0	1	1	1
0	1	1	0	0
1	0	0	1	0
1	1	0	0	0

↑ result: same as NOR ↑

⇒ $\bar{A} \cdot \bar{B} = \overline{A + B}$

Digital Chips

Part no.


74 LS 02

it's a digital chip

TTL


"Quadruple 2-input NOR gate"

Pin Diagram

 


Design reminder

 It is OK to connect one output to multiple inputs



↑ OK: two inputs connected to one output

 
It is NOT OK to connect multiple outputs together



"Fanout"

When one circuit's output drives multiple inputs, that's called "fanout"

ex. "Fanout of 3"

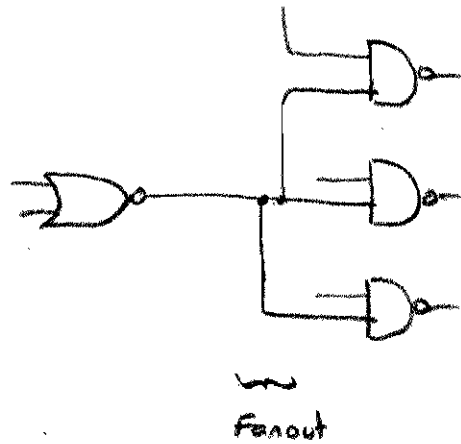

A digital gate can typically source/sink enough current for a fanout of 10 or more

DRIVING LEDs



many student projects use LEDs

it's easy to use too many LEDs

because an LED is a big power consumer

a gate can drive one LED

  
if you need to drive more, use a transistor switch



How to use another gate as an inverter

recall NAND truth table

A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

 


note Δ always use a resistor when connecting a digital input directly to 5V

input	output
B	Q
0	1
1	0

inverter

multiplexer concept

 
you'll use in Lab 8 - it's like a switch to choose an input




one output, the same as the input that is specified by the "data select input"

Mechanical Switches

a user interface to enter data

 

the only trouble with this is "bounce"

 

cure for bounce later in LAB 9.

Binary - Coded Decimal

LAB 9


Four binary bits:

- called A, B, C, D
- represent numbers from 0 to 9

* <u>count</u>	<u>D</u>	<u>C</u>	<u>B</u>	<u>A</u>
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1

Divide-by-10 Counter (LAB 9)

One use: reduce frequency by 10

 

Another use:

use 4 outputs D C B A

which advance (as in * above) at each clock input



when it gets to 9, it starts again at 0,
(like a digit in car odometer)



One-Shot

LAB 10

aka "monostable multivibrator"

a device widely used to:

  - produce a trigger pulse
- produce a pulse of a desired duration
- analog-to-digital conversion




start of pulse is triggered when input crosses threshold


↔ pulse width determined by external RC

one-shot (cont.)

 
In LAB 10, you will convert an analog input (sine wave) to a digital output (pulse train) using a one-shot



Digital clocks (clk)

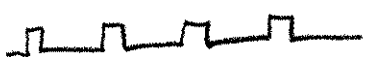- a pulse train 
- used by digital circuits that involve:
 - timing
 - transferring data

terminology:

 

Flip Flops

Flip flops are digital devices that:

- have memory
- have two stable states

which state the flip-flop has depends on previous history — this is related to the concept of "memory"


Types of flip-flops:

- SR = set reset, the simplest flip-flop
- Clocked Flip Flops:
 - D = data flip flop, these are often combined to make a "shift register"
 - JK has two data inputs; otherwise much like a D flip flop

Here, we will focus on how an S-R flip-flop functions. In the lab you will also use D and JK flip flops.

SR (Set-Reset) Flip Flop

Has two data inputs, no clock input

 

↑
inputs


↑
outputs

recall NAND truth table:

inputs		output
0	0	1
0	1	1
1	0	1
1	1	0


↑
don't erase
from blackboard

How it is used:

- inputs A & B are usually HIGH (and the flip-flop outputs will be in one of two possible stable states)
- one input is momentarily made LOW  to SET or RESET the outputs.

first stable state

 suppose inputs $A \& B$ are HIGH & output X is HIGH
what is output Y ?



examine the NAND truth table (previous page)

for the lower NAND gate



both inputs are HIGH, i.e. 1

\Rightarrow output must be LOW


$\Rightarrow Y=0$

so, if $A \& B$ are HIGH and X is HIGH
then Y must be LOW

second stable state

suppose inputs $A \& B$ are HIGH & output X is LOW
what is output Y ?

 again, examine NAND truth table
for the lower NAND gate



NAND truth table $\Rightarrow Y=1$

so, if A & B are HIGH & output X is LOW
then Y must be HIGH

summary of the two stable states:

- when both inputs A, B are HIGH,
there are two stable states of the
output X, Y

first: $X=1, Y=0$

second: $X=0, Y=1$


- Q: which of these two states will
it be in?

A. For flip-flops in general, this
will depend on the history of
previous inputs applied to the
flip flop. For the SR flip flop,
it depends on whether an input
has been "RESET"


reset for SR flip-flops

Suppose the SR flip flop is initially in
the stable state: inputs $A=B=1$
outputs $X=1, Y=0$

Next, let's bring B to low momentarily

 

After step 1, the inputs look like this:

 

To find outputs X & Y , let's start by
asking "can X be HIGH?"

If X is HIGH, then the lower
gate looks like




which is not allowed (see
NAND truth table)

- $\Rightarrow X$ cannot be HIGH
- $\Rightarrow X$ must be Low

Thus, after step 1, the inputs are $A=1, B=0$
 outputs are $x=0, y=1$ *

note: output state is now
 opposite of what it
 was before step 1

After step 2

 

bring B back to high

- The outputs after step 1 (* above) were $x=0, y=1$

Now we also have $A=1, B=1$

- This combination $A=1, B=1$ inputs $x=0, y=1$ outputs is one of the two stable states.

- So the outputs do not change in step 2

Summary for SR flip flop "reset":

Usually you keep both inputs high.

If you momentarily bring input B Low, then back to HI, that will "reset" the flip-flop to the state $x=0, y=1$. (If it was already in that state, then nothing changes.)


Timing Diagram (general)

In digital electronics, we need "truth tables" for gates, and for flip-flops (& other devices that involve timing or memory) we also need "timing diagrams"

discuss: [for special projects: timing diagrams, unlike schematic diagrams, are not graded, but they might help you in designing your project & debugging it

Timing Diagram

 SR flip flop (showing it "resetting" when input B is brought low).



The other possibility for resetting the SR flip flop is to bring input A low, (instead of input B). This will reset the flip flop to state $X=1, Y=0$

Latches


another name for SR flip flop,

Application of SR flip flops

switch debouncing

(text p. 506 & lab 9)

Data D-flip flop (as in lab 9)

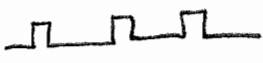
- is a clocked flip flop
- clock input is a train of pulses

- indicated on chip with an arrow >



 
 inputs outputs

- also has CLR input to "CLEAR" state of flip flop (CLR=1 forces Q→1)
- requires +5V, GND power supply

 
what's inside a D-flip flop



timing:





<p>causes master flip to do something: M goes to the state of input D</p>	<p>causes slave flip flop to do something: output Q goes to the state of M</p>
---	--

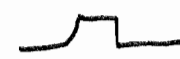so after one clk pulse  the data (0 or 1) that was on input D is transferred to output Q

Applications of D flip-flop:

Shift Register (Lab 9)

 

at each clk pulse 
 the data in the register (a sequence of 1's & 0's) shifts to the right.

useful for serial memory

Divide-by-2 Counter

