

Opto electronics

①

= light sources & light detectors
textbook section 9.10

Applications of opto-electronics

indicators

- LED shows ON/OFF
or OK/NOT-OK
on front panel of
your instrument


↙ oral story:
paddle wheel switch → LED
indicate water
flow & interlock status in
high-power
scientific instrument
like a laser

displays

- digital display, like
calculator
- in lab you use
7-segment LED display

isolation

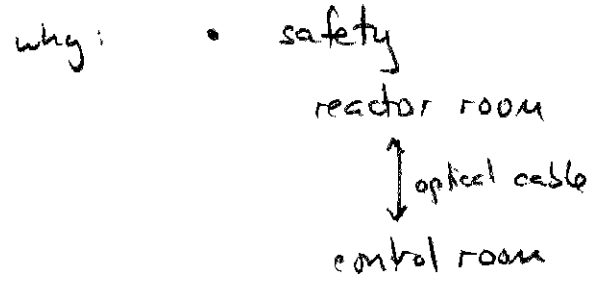electrically isolate two circuits by sending signal optically




- separate power supplies

show viewgraphs:

- pulser circuit for electron beam
- data sheet page for optoisolator

fiber-optic transmission

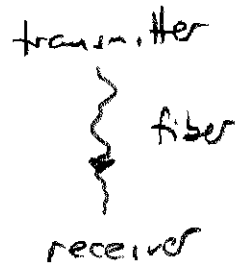


- why:
- avoid noise pickup
 - long-distance data transmission
- oral story: thesis project

Optoelectronic devices

- semiconductors (typically GaAs & similar, not Si)
 - Laser diode
 - LED
 - photodiode
 - phototransistor
 - CCD or CMOS imaging
- VACUUM
 - PMT (photo multiplier tube)

LEDs

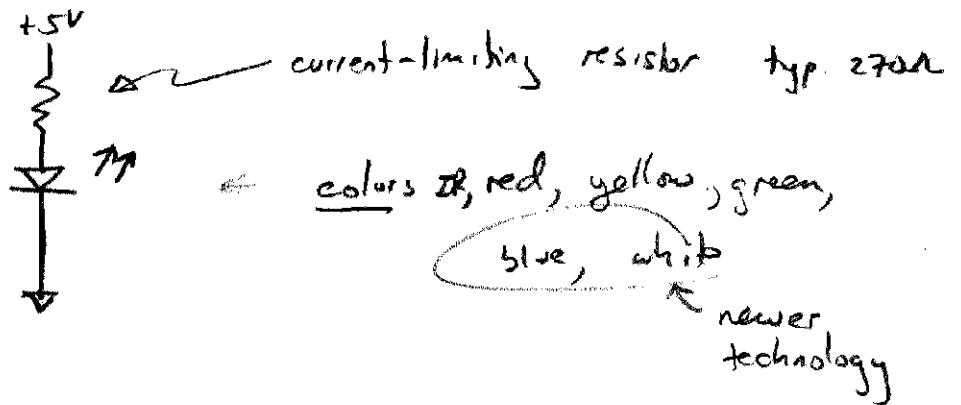

packages

- for front panel, use a "bezel" to mount in hole
- arrays of LEDs for bargraph indicator

limiting resistor: determines current consumption

$$I = \frac{V}{R}$$

$$= \frac{5V}{270\Omega}$$

$$= 18\text{ mA}$$

↑
a lot, especially
if you use lots of
LEDs

speed


you measured rise time
> 30 nsec in Lab 6

Laser diode

looks similar to LED, but:

- more monochromatic
- switches ON/OFF much faster (nsec)

just provide a power supply

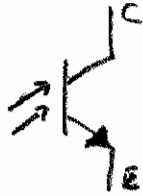
Photo transistor

like an npn transistor, except:

- transparent case
- light hits base-collector junction & photons generate electron current at base
- more light \Rightarrow more base current

speed:

you measure rise time $\sim 4 \mu\text{s}$
in Lab 6

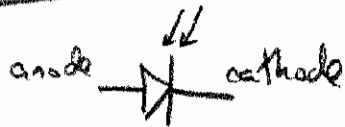Photodiode

photon excites electron in pn junction, then electron flows to cathode

so light \Rightarrow current

compare:

	photo transistor	photo diode
<u>different</u>	has current gain	no current gain
	slower (μs) response time	faster (~ nsec)
min:	minimum detectable light level is about the same	

photodiode use:


- zero bias ⇒ photovoltaic mode
used for solar cells
- reverse bias ⇒ photoconductive mode
provides fast rise time
for detecting signals

• avalanche

big reverse bias

⇒ electrons multiplied by
"avalanche breakdown"

⇒ ...

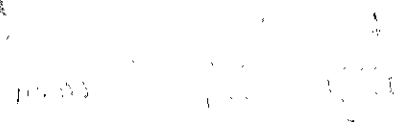

detector terminology:


"responsivity" = ratio of $\frac{\text{generated photocurrent}}{\text{incident light power}}$

"quantum efficiency" = ratio $\frac{\text{number of photo-generated electrons}}{\text{number of incident photons}}$

dimensionless quantity,
typically ~ 10%

PMT photomultiplier tube

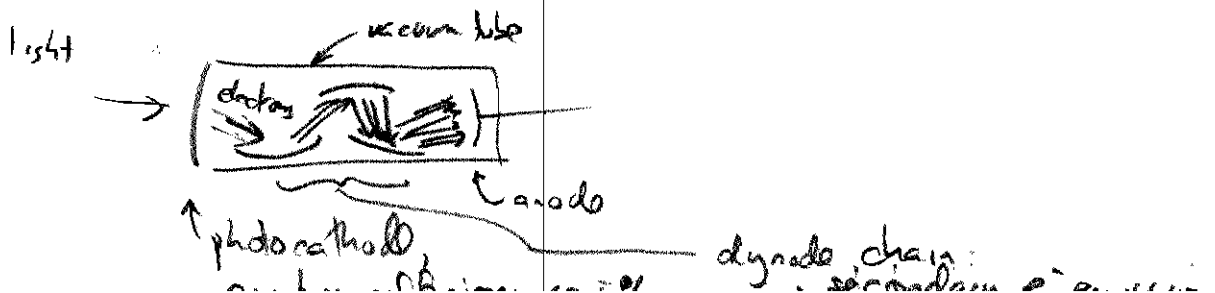
- a competitor to avalanche photo diode
- fast (~ nsec)
- efficient
- requires HV "supply" (like avalanche photodiode)
- applications:
 - particle physics scintillation detector
 - spectroscopy labs



Opto isolators

package with LED & photo transistor
in same package

ex 4N35

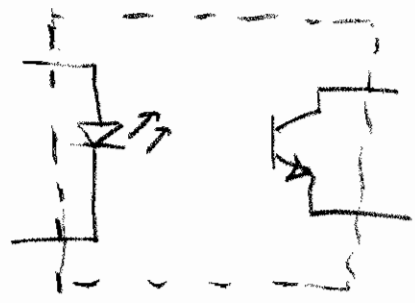


show wavegraphs

- pulser circuit for e-beam

example circuit

- data sheet for opto isolator

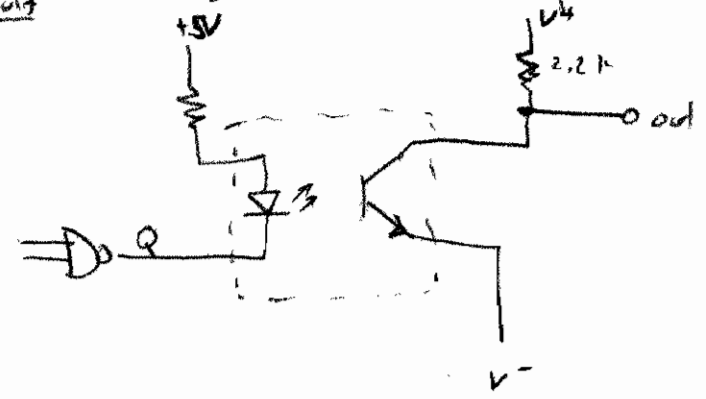

digital circuit,
uses a 5V
supply


analog circuit,
uses different
power supply

in this example:

- when Q is HI

LED is OFF

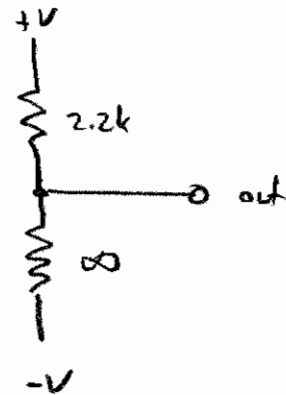→ no base current in transistor
 right half of circuit looks like:




so output voltage is +V

- when Q is LO

LED is ON

→ lots of base current in transistor
 → transistor conducts

right half of circuit looks like

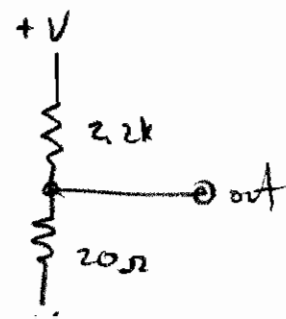

so output voltage is $\approx -V$ →